

LAB ASSIGNMENT – 3

Course: Basic Electrical and Electronics Engineering

Course Code: EEE1001

Faculty Name: Prof. Medaramelta Praveenkumar

Slot: L-19+L-20

Name: Priyal Bhardwaj

Registration Number: 18BIT0272

Submission Date: 14.09.2018

Ex. No.:2

Date: 14.09.2018

Verification of NETWORK THEOREMS (Maximum Power Transfer Theorem)


Aim:

Apparatus/Tool required:

ORCAD / Capture CIS --> Analog Library – R,
Source Library – Vdc, Idc &
Ground (GND) – 0 (zero)

Simulation Settings: Analysis Type - Bias Point

Circuit Diagram

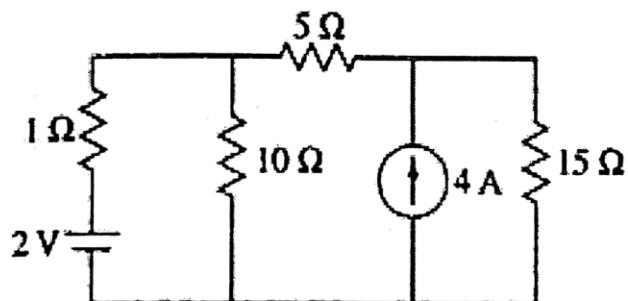


Statement: Maximum Power Transfer Theorem

The theorem states that "maximum power is transferred from the source to the load when the load resistance (R_L) is equal to the Thvenin's equivalent resistance (R_{th})".

Manual Calculations:

To Find V_{th} :

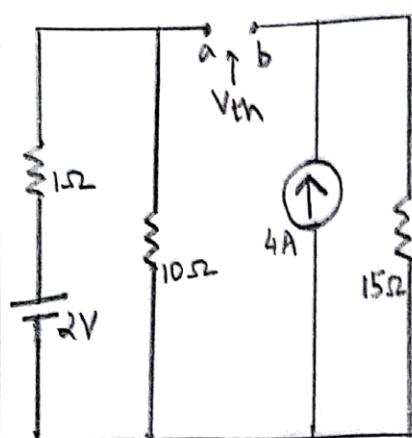


$$V_{th} = V_a - V_b$$

$$V_a = \frac{2 \times 10}{11} = 1.818 \text{ V}$$

$$V_b = 60 \text{ V}$$

$$V_{th} = V_a - V_b = 58.182 \text{ V}$$

To Find R_{th} :

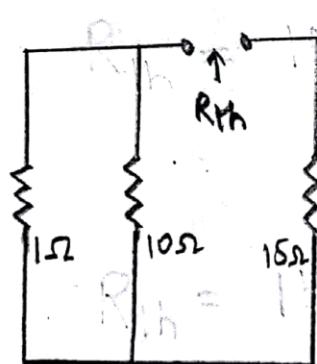

1Ω & 10Ω in parallel
 1Ω & 15Ω is in series

$$\rightarrow R_{th} = 15 + \frac{10 \times 1}{10 + 1}$$

$$R_{th} = 15.91 \Omega$$

$$R_{th} = 15.91 \Omega$$


To Find Power:

$$P_{max} = \frac{(V_{th})^2}{4R_{th}} = \frac{58.182 \times 58.182}{4 \times 15.91}$$

$$P_{max} = 53.19 \text{ W}$$


Simulation Circuit:

To Find V_{th} :

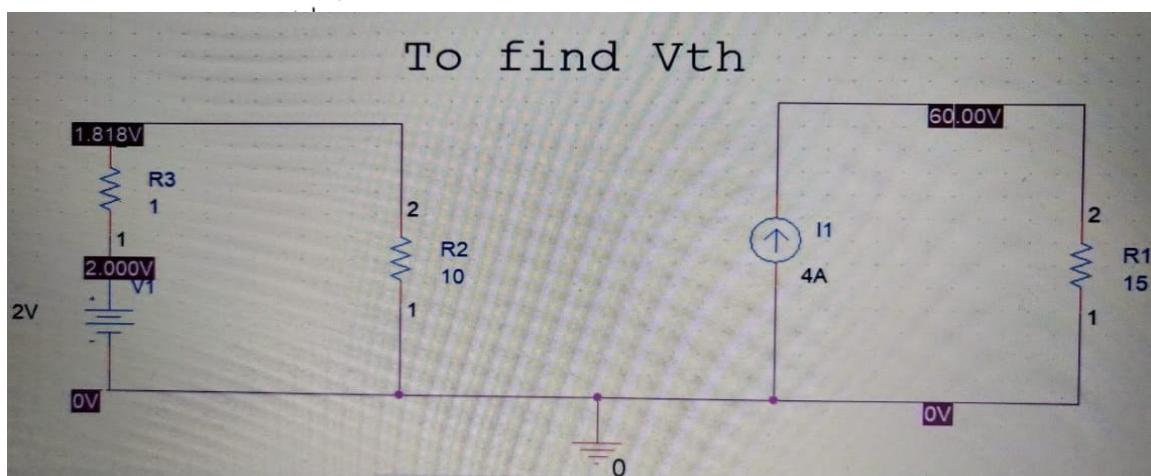


$$V_{th} = 60 - 1.818 = 58.182 \text{ V}$$

To Find R_{th} :

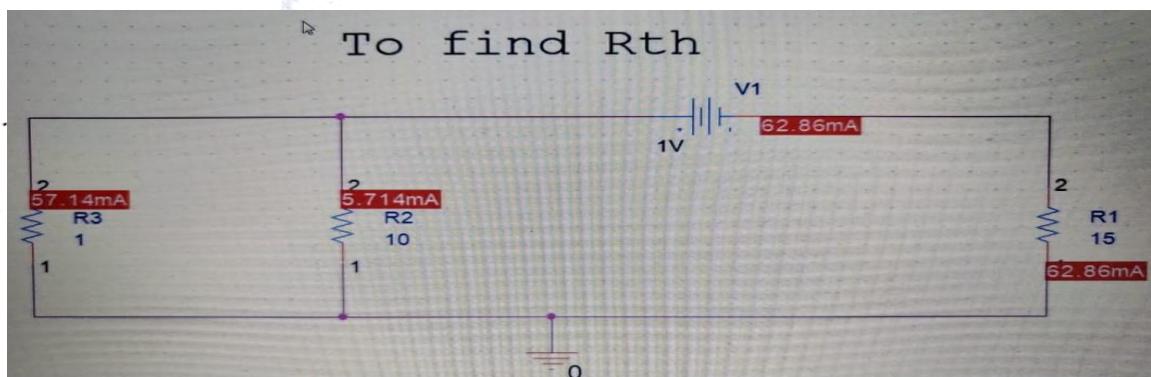

$$R_{th} = \frac{1}{62.86 \text{ mA}} = \frac{1000}{62.86} = 15.908 \approx 15.91 \Omega$$

To Find Power:

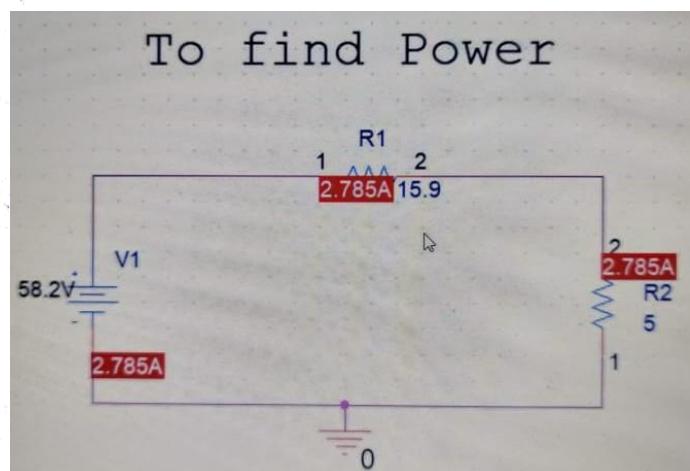

$$I_L = 2.785 \text{ A}$$

Procedure:

- 1) Construct the circuit given.
- 2) To find V_{th} , remove load resistance, replace current & voltage sources with open circuit & short circuit respectively (Nodal Analysis).
- 3) Mark the ends as A & B (of removed load resistance).
- 4) Thvenin's Resistance (R_{th}) is equal to resistance across A & B.
- 5) Using KVL, find Thvenin's voltage which is equal to $V_B - V_A$.
- 6) Now find power for the different resistances by simulation.
- 7) From the theorem & Power formula; Maximum Power obtained (P_{max}) = $\left[(V_{th})^2 / 4R_{th} \right]$.
- 8) Check whether manually calculated results are equal to simulated results.

Result:

Maximum Power Transfer Theorem

Manual Calculations

$$V_{th} = 58.182 \text{ V}$$

$$R_{th} = 15.91 \Omega$$

$$P_{max} = 53.19 \text{ W}$$

Simulated Result

$$V_{th} = 58.182 \text{ V}$$

$$R_{th} = 15.91 \Omega$$

$$P_{max} = 53.19 \text{ W}$$

Inference:

Since Simulated values = Manual calculations,
Maximum Power Transfer Theorem is verified.

SIMULATED CIRCUIT & GRAPH

