

LAB ASSIGNMENT – 2

Course: Basic Electrical and Electronics Engineering

Course Code: EEE1001

Faculty Name: Prof. Medaramelta Praveenkumar

Slot: L-19+L-20

Name: Priyal Bhardwaj

Registration Number: 18BIT0272

Submission Date: 30.08.2018

Ex. No.:3

Date:

Response of RLC Series Circuit


Aim: For the given RLC circuit find the resonant frequency and verify it using simulation.

Apparatus/Tool required:

ORCAD / Capture CIS --> Analog Library – R, L & C
Source Library – Vac
Ground (GND) – 0 (zero)

Simulation Settings: Analysis Type – Transient (Time Domain)
Run to time: 20ms

Circuit Diagram:

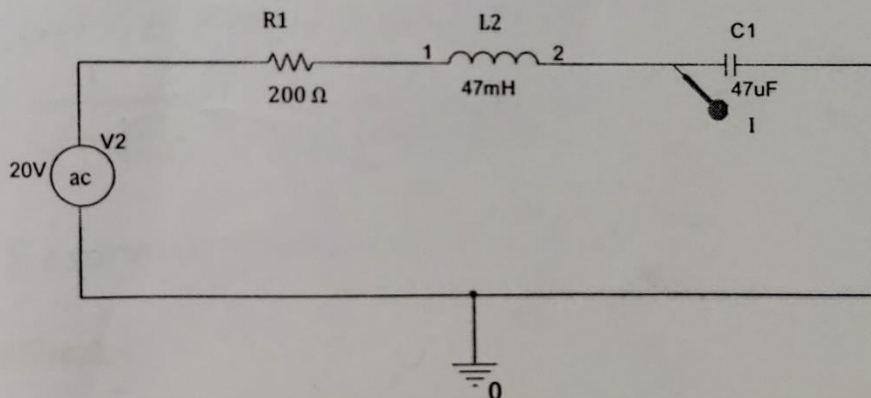

Theory: When the resistor, capacitor and inductor are connected in series forming a series RLC circuit, it is seen that resonance occurs in circuit when the supply frequency causes the voltage across L and C to be equal and opposite in phase.

Formulae :

Inductive Reactance; $X_L = \omega L = 2\pi fL$

Capacitive Reactance; $X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$

Total Impedance; $Z = R + j\omega L + \frac{j}{\omega C}$

$$\Rightarrow |Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

• When $X_L = X_C \rightarrow \text{Resonant Frequency} = \frac{1}{2\pi\sqrt{LC}}$

Calculation:

$$X_L = X_C \rightarrow 2\pi fL = \frac{1}{2\pi fC} \rightarrow f^2 = \frac{1}{4\pi^2 LC}$$


$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

Resonant Frequency (when $X_L = X_C$):


$$= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{47 \times 47 \times 10^{-9}}} = \frac{10^4 \times \sqrt{10}}{2\pi \times 47} = 107.13 \text{ Hz}$$

$\Rightarrow \text{Resonant Frequency} = 107.13 \text{ Hz}$

Model Graph:

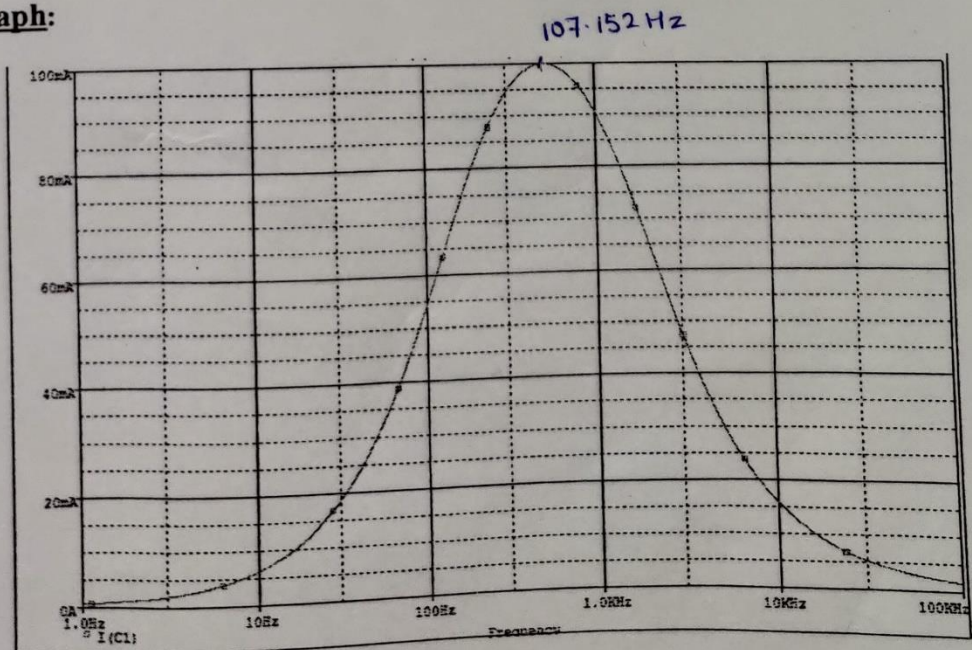

Simulation Circuit Diagram and Output:

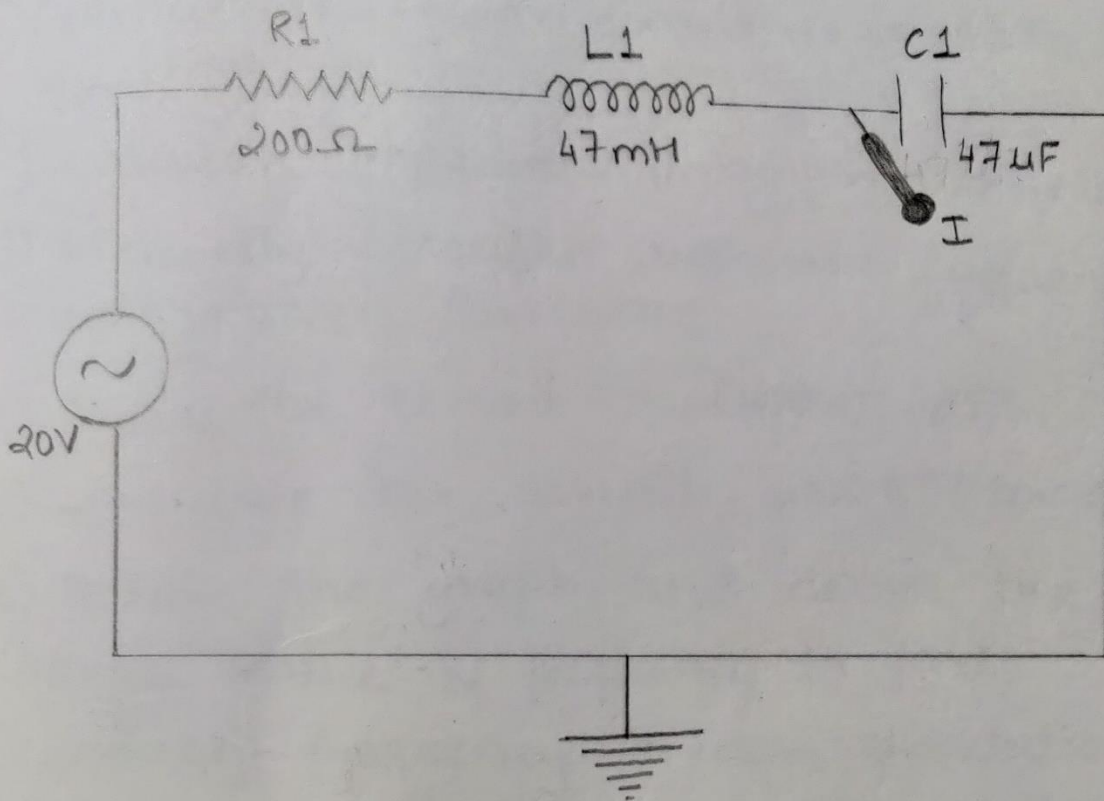

$$\begin{aligned}
 X_L &= 2\pi fL \\
 &= 2 \times 3.14 \times 47 \times 10^{-3} \times f \\
 &= 0.295 f
 \end{aligned}$$

$$\begin{aligned}
 X_C &= \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 47 \times 10^{-6} \times f} \\
 &= \frac{10^6}{295.16 f} = \frac{3387.99}{f}
 \end{aligned}$$

Output :-

f (Hz)	I (mA)
1	5.896
10	51.185
100	99.97
107.152	100
1000	56.52
30000	2.2775

Procedure:-

- 1) Construct the same circuit as mentioned in the question.
- 2) Calculate impedance using given formula.
- 3) Manually calculate resonant frequency using given formulae.
- 4) Place the circuit in Capture CIS.
- 5) Simulate the circuit using Pspice.
- 6) Obtain the graph and derive the peak value of frequency to find resonant frequency through simulation.
- 7) Note down your observations

Result:- Resonant frequency by :-

- (1) Manual Calculation - 107.13 Hz
- (2) Simulation - 107.152 Hz



\Rightarrow Manual \approx Simulation

$$\text{Difference} = 107.152 - 107.130 = 0.022 \text{ Hz}$$

Maximum current (I_{max}) at resonant frequency = 100 mA

Inference:- Calculated & simulated results are similar and hence resonant frequency is determined correctly, when $X_L = X_C$.

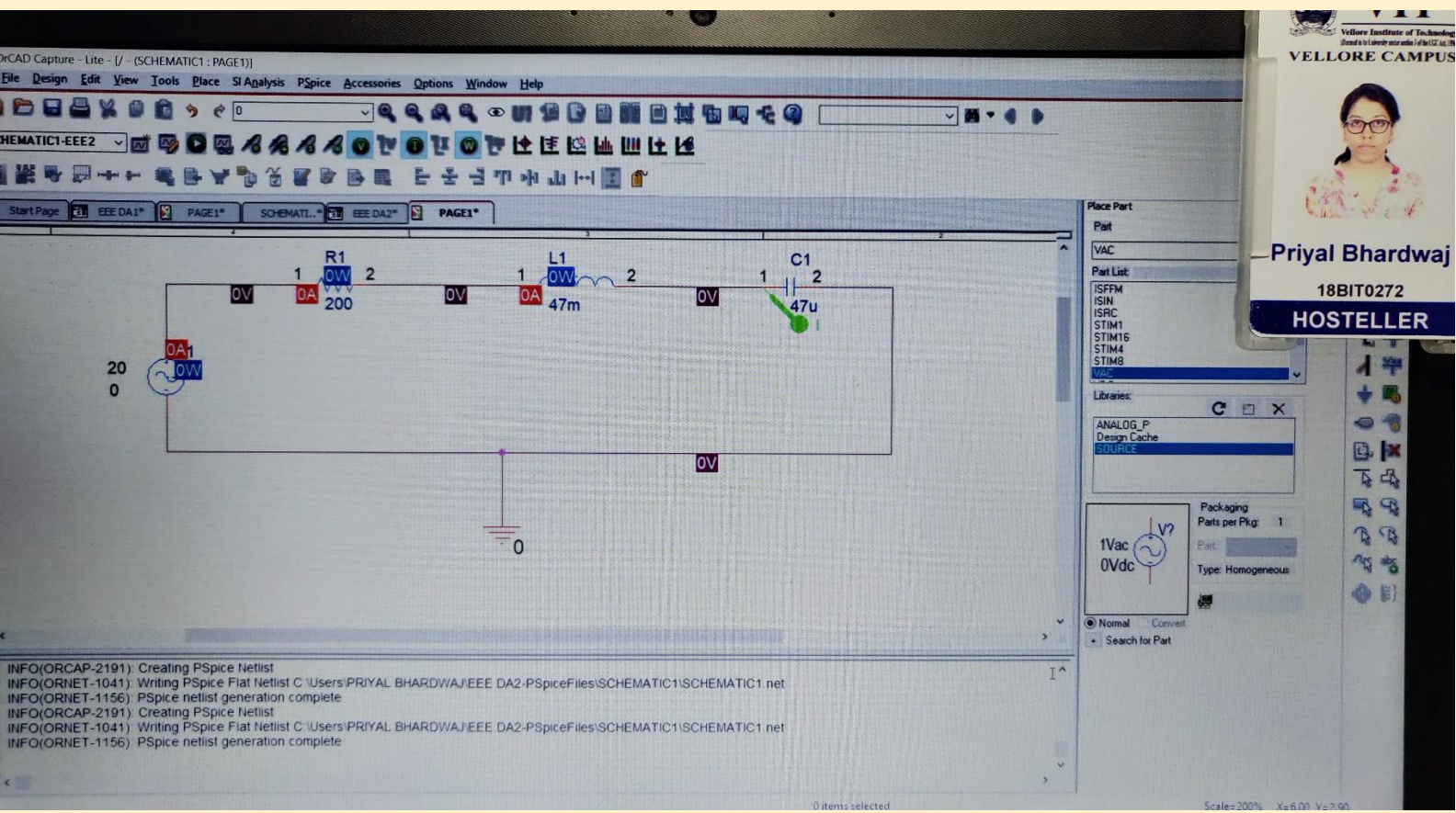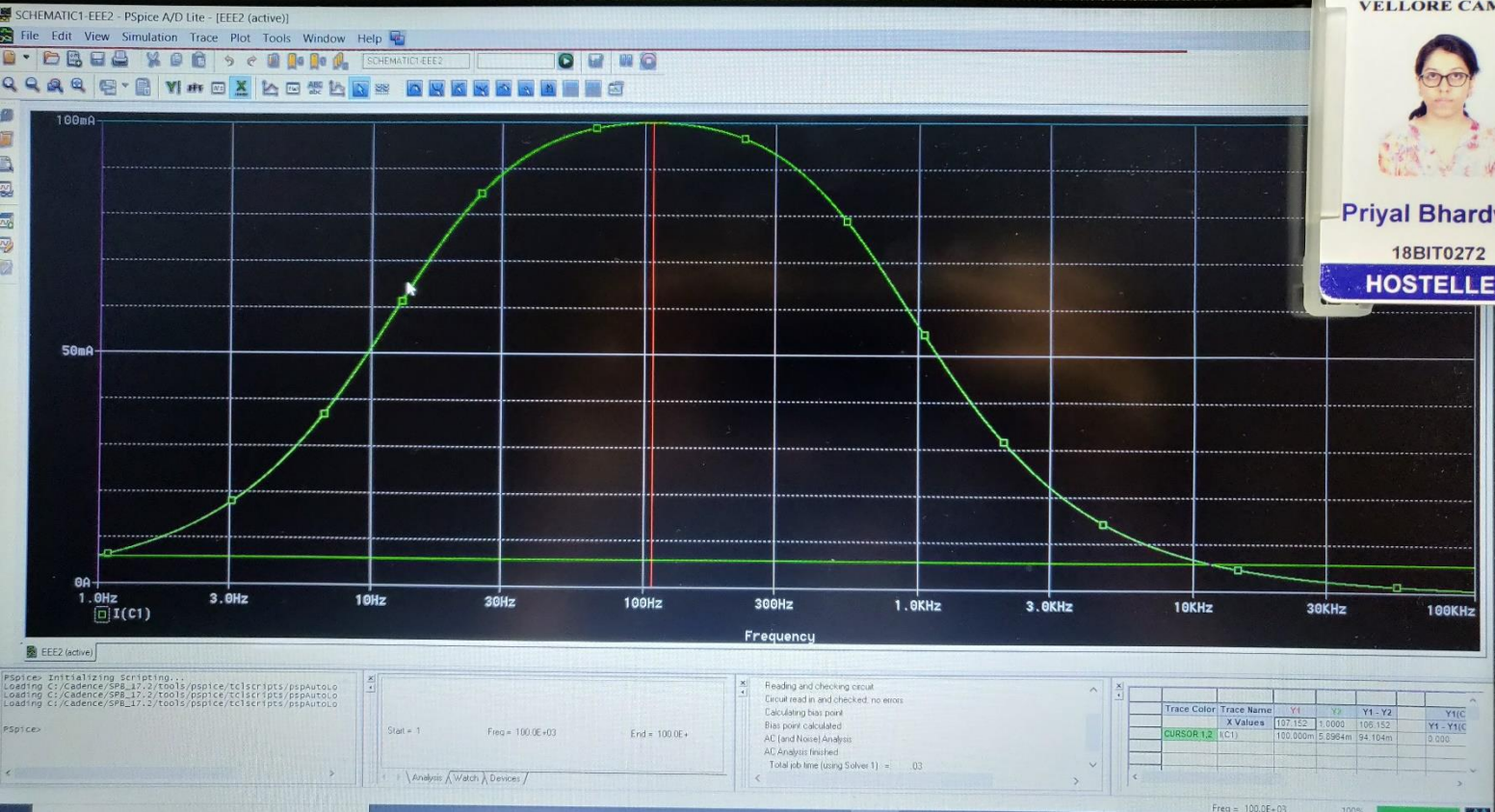Reg. No: 18BIT0272 Name: PRIYAL BHARDWAT Date: 30/08/2018



Priyal Bhardwaj

18BIT0272

HOSTELLER