

## **LAB ASSIGNMENT – 10**

**Course:** Basic Electrical and Electronics Engineering

**Course Code:** EEE1001

**Faculty Name:** Prof. Medaramelta Praveenkumar

**Slot:** L-19+L-20

**Name:** Priyal Bhardwaj

**Registration Number:** 18BIT0272

**Submission Date:** 13.11.2018

Ex. No.:4

Date: 25/10/2018


## Design of Half Adder Circuit using gates

Aim: Implement & verify half-adder circuit.

Apparatus Required:

S. No.	Name of the apparatus	Range / Type	Quantity
1	7486 gate	-	1 No.
2	7408 gate	-	1 No.
3	LED	-	2 Nos.
4	RPS	0 - 15 V	1 No.
5	Resistor	330 $\Omega$	2 Nos.
6	Breadboard	-	1 No.
7	Wires	-	Few

Circuit Diagram:

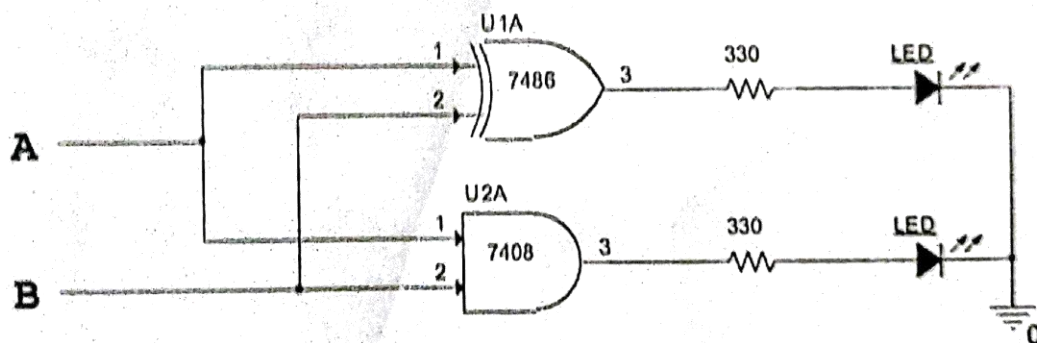


Theory:

Circuit needs 2 binary inputs & 2 binary outputs. The input variables designate the augend and addend bits; the output variables produce the sum & carry. The truth table is listed.

Sum represents output of XOR gate and carry represents output of AND gate.

**PRACTICAL CIRCUIT: -**

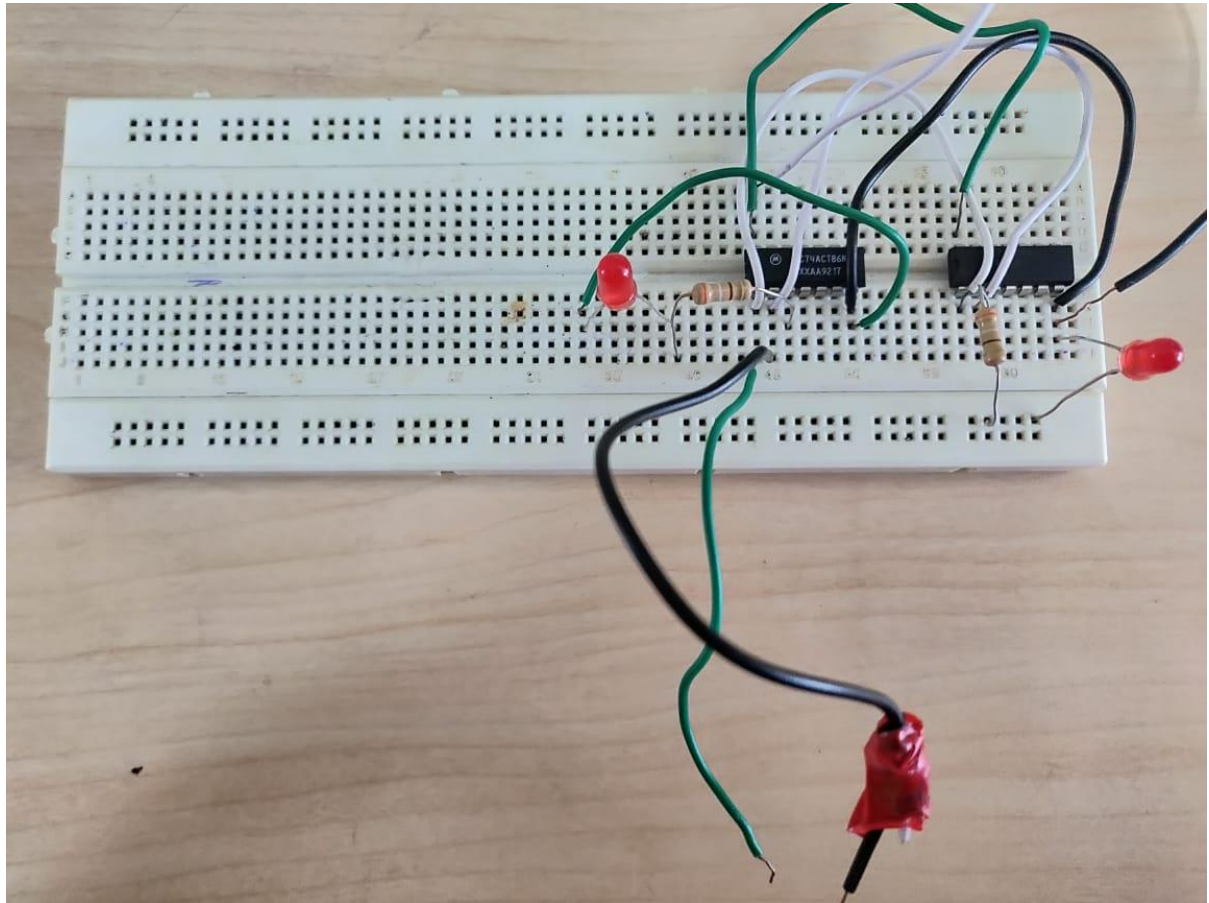



Truth Table

A	B	$S = A \oplus B$	$C = A.B$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$C = AB$$

**Observation:**

It is observed that on giving the inputs the LEDs glow in accordance with the truth table thus verifying the implemented circuit.

**Procedure:**


- 1) Connect the XOR & AND gates along with the LEDs, source & wires to the breadboard according to the given circuit. Switch on voltage source.
- 2) Give the inputs according to truth table by connecting wires to ground (7) for 0 & to (14) for 1 input.
- 3) Record your observations

**Result:**


Truth table is verified using logic gates for half-adder.

Reg. No: 18BIT0272 Name: PRIYAL BHARDWAJ Date: 13/11/2018

A	B	S	C
0	0	0	0

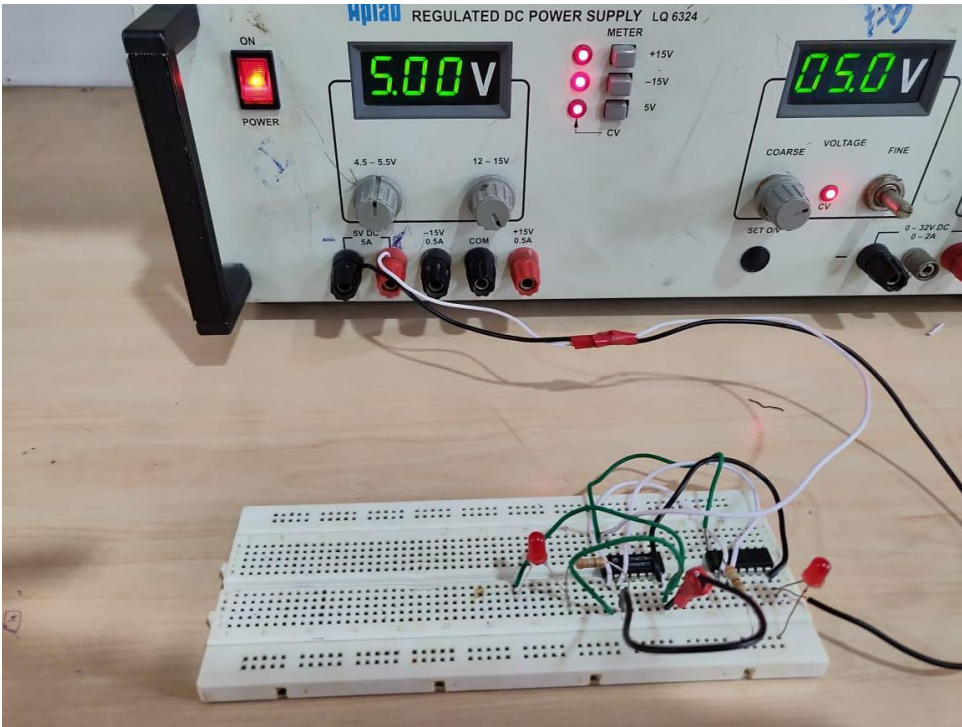


A	B	S	C
0	1	1	0

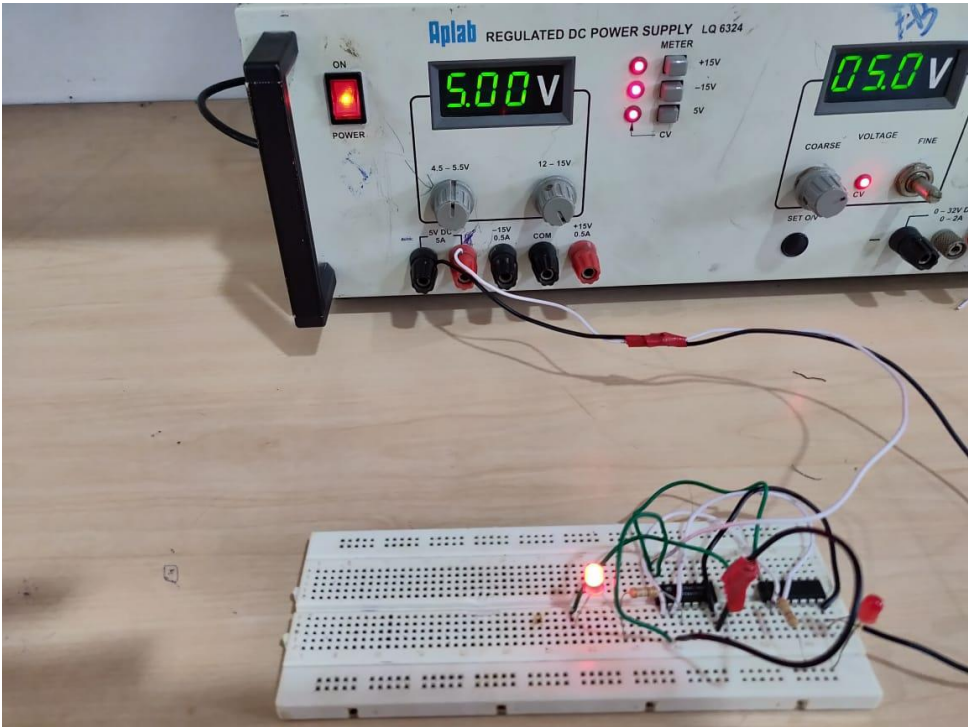



A	B	S	C
1	0	1	0

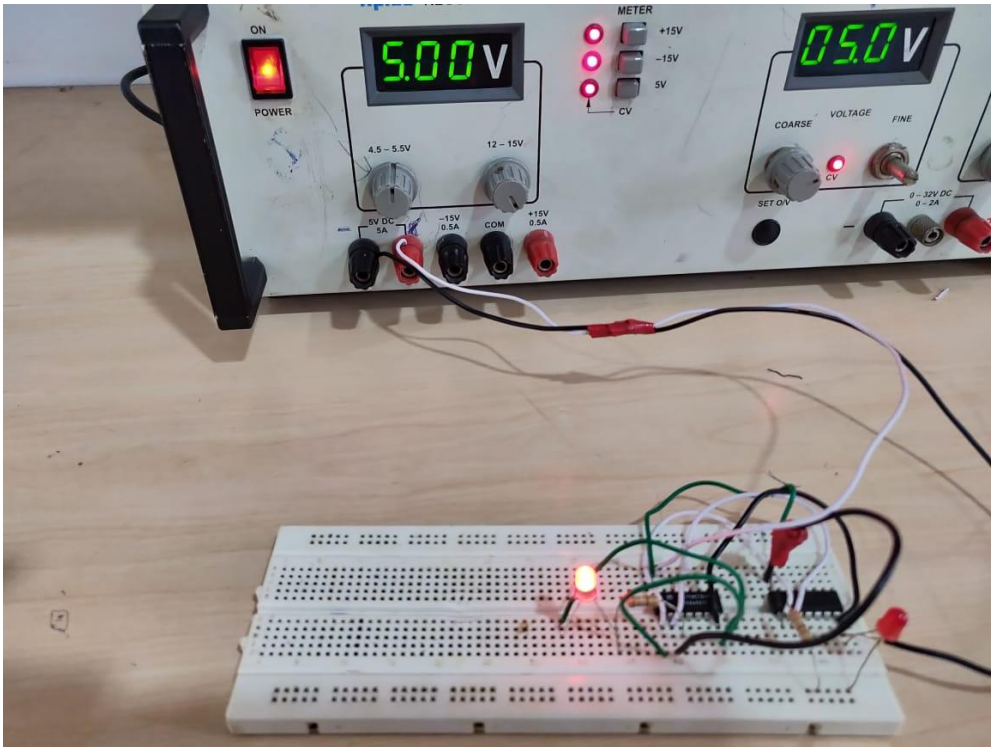

A	B	S	C
1	1	0	1

