

LAB ASSIGNMENT – 9

Course: Basic Electrical and Electronics Engineering

Course Code: EEE1001

Faculty Name: Prof. Medaramelta Praveenkumar

Slot: L-19+L-20

Name: Priyal Bhardwaj

Registration Number: 18BIT0272

Submission Date: 13.11.2018

Ex. No.: 1

Date: 13/11/2018


Verification of KIRCHHOFF'S LAWS (Mesh and Nodal Analysis)

Aim: Verify nodal & mesh analysis for the given circuit.

Apparatus/Tool required:

SL No.	Components Name	Range	Quantity
1	Resister	330Ω, 270Ω, 390Ω, 220Ω, 180Ω	Each 1 No.
2	Ammeter	0-50mA (DC)	1 No.
3	Voltmeter	0-30V (DC)	1 No.
4	RPS	0-32 V (DC)	1 No.
5	Connecting Wires	-	Few
6	Bread Board	-	1 No.

Circuit Diagram:

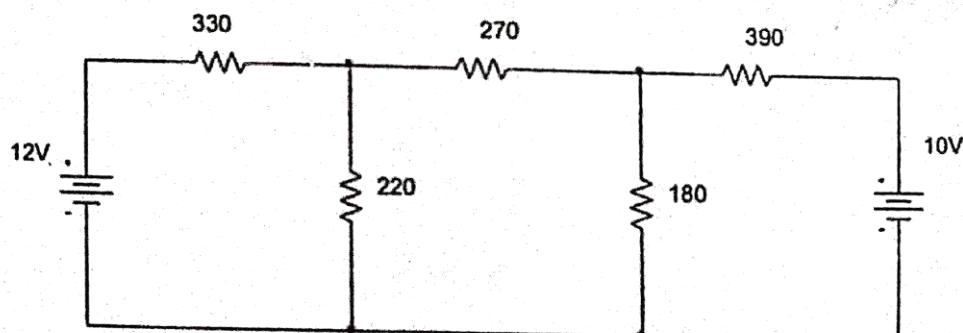

Theory:

Kirchhoff's Current Law (KCL):


It deals with the conservation of charge i.e. entering & leaving currents are equal.

Kirchhoff's Voltage Law (KVL):

The algebraic sum of the products of the resistances of the conductors & the currents in them in a closed loop is equal to the total emf available in the loop.

Practical Circuit and output:

Mesh Analysis:

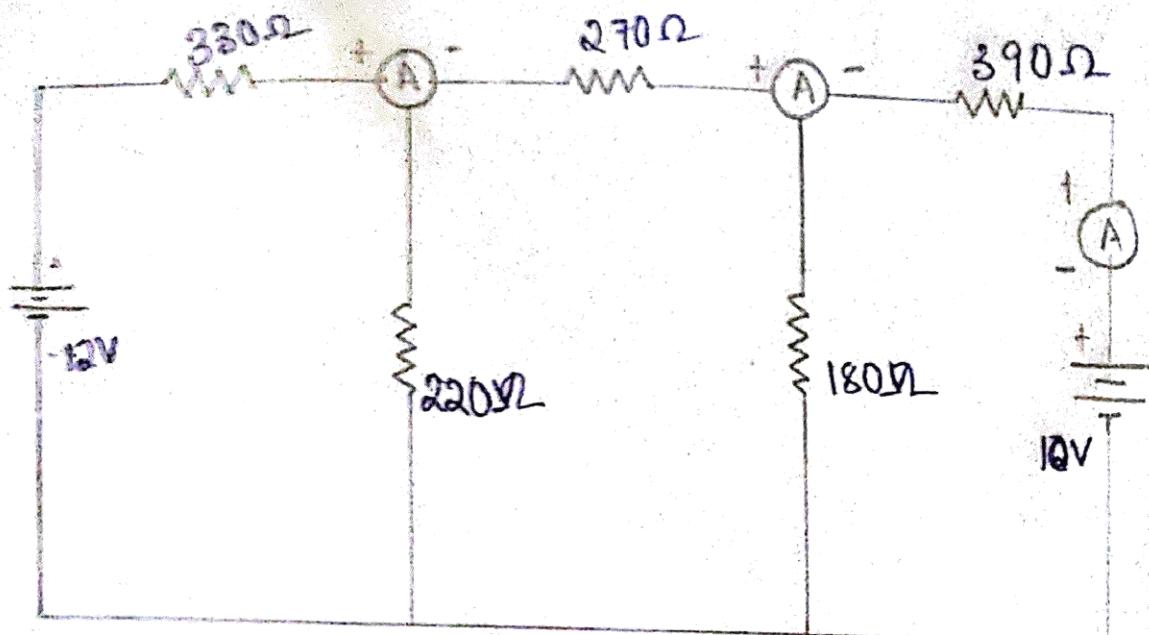

where i_1 , i_2 , i_3 are the loop currents.

$$i_1 = 23.069 \text{ mA}$$

$$i_2 = 3.1269 \text{ mA}$$

$$i_3 = -16.556 \text{ mA}$$

KVL for loop 1

$$-12 + 330i_1 + 220(i_1 - i_2) = 0$$

$$550i_1 - 220i_2 = 12 \quad \text{--- (1)}$$

KVL for loop 2

$$270i_2 + 180(i_2 - i_3) + 220(i_2 - i_1) = 0$$

$$22i_1 - 67i_2 + 18i_3 = 0 \quad \text{--- (2)}$$

KVL for loop 3

$$390i_3 + 10 + 180(i_3 - i_2) = 0$$

$$18i_2 - 57i_3 = 1 \quad \text{--- (3)}$$

From (1), (2) & (3)

$$i_1 = 23.069 \text{ mA}$$


$$i_2 = 3.1269 \text{ mA}$$

$$i_3 = -16.556 \text{ mA}$$

Practical Circuit & Output

Manual Calculations:

Nodal Analysis

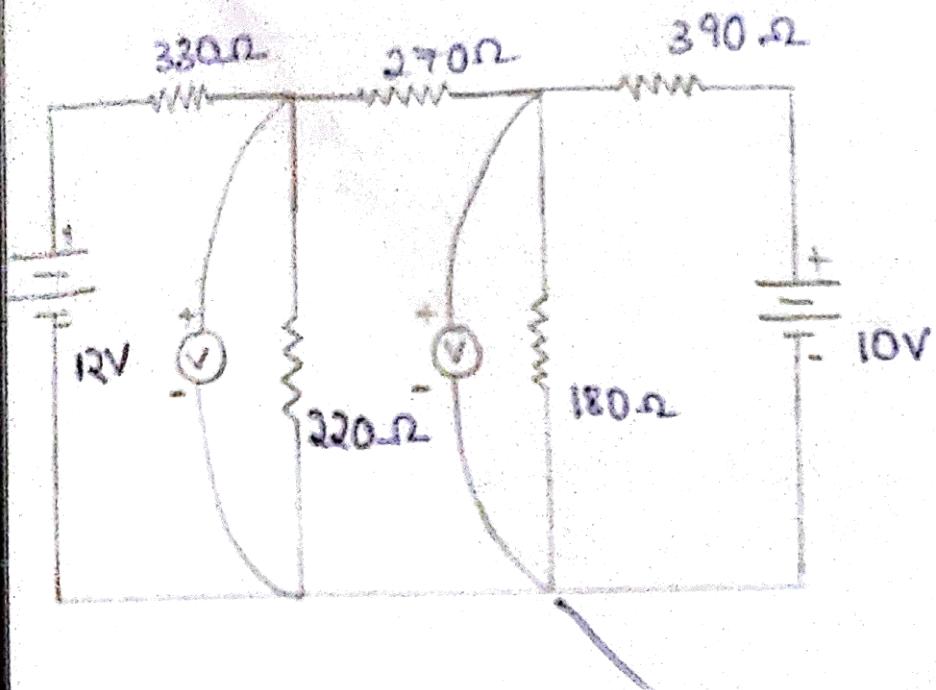

$$V_1 =$$

$$V_2 =$$

NOTE: -

For NODAL Analysis practically circuit was not implemented in class, hence only manual calculations done.

manual Calculations

Node Analysis:

Applying KCL at node A :

$$i_1 = i_2 + i_3$$

$$\frac{12 - V_A}{330} = \frac{V_A - 0}{220} + \frac{V_A - V_B}{270}$$

$$67V_A - 22V_B = 216 \quad \text{--- (1)}$$

Applying KCL at node B :

$$i_3 = i_4 + i_5$$

$$-(V_B - V_A) = \frac{V_B - 0}{180} + \frac{V_B - 10}{390}$$

$$26V_A - 83V_B = -180 \quad \text{--- (2)}$$

On solving (1) & (2)

$$V_A = 4.387V$$

$$V_B = 3.543V$$

Procedure:

- 1) Find the value of each resistor before fixing them on the breadboard.
- 2) Connect all other components as per the circuit diagram.
- 3) Switch the current or voltage source as per the requirement.
- 4) Using the coarse & fine settings set the voltage as 10V & 12V & find the voltage across the resistors.

Result:

Mesh Analysis:

Manual Calculations

$$i_1 = 23 \text{ mA}$$

$$i_2 = 3 \text{ mA}$$

$$i_3 = 16.55 \text{ mA}$$

Practical output

$$i_1 = 23 \text{ mA}$$

$$i_2 = 3 \text{ mA}$$

$$i_3 = 16.5 \text{ mA}$$

Node Voltage Analysis:

Manual Calculations

$$V_A = 4.3 \text{ V}$$

$$V_B = 3.5 \text{ V}$$


Practical output

Inference:


Thus by using KVL we can solve mesh analysis

Reg. No: 18B1T0272 Name: PRIYAL BHARDWAJ Date: 13/11/2018

1. I1

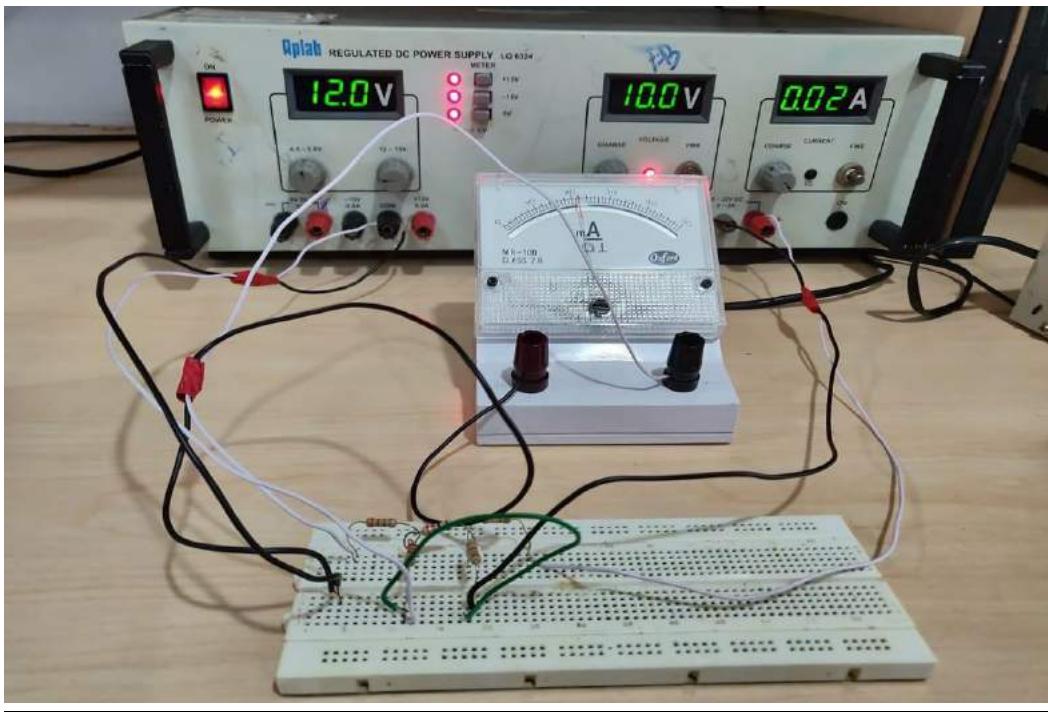

2. I2

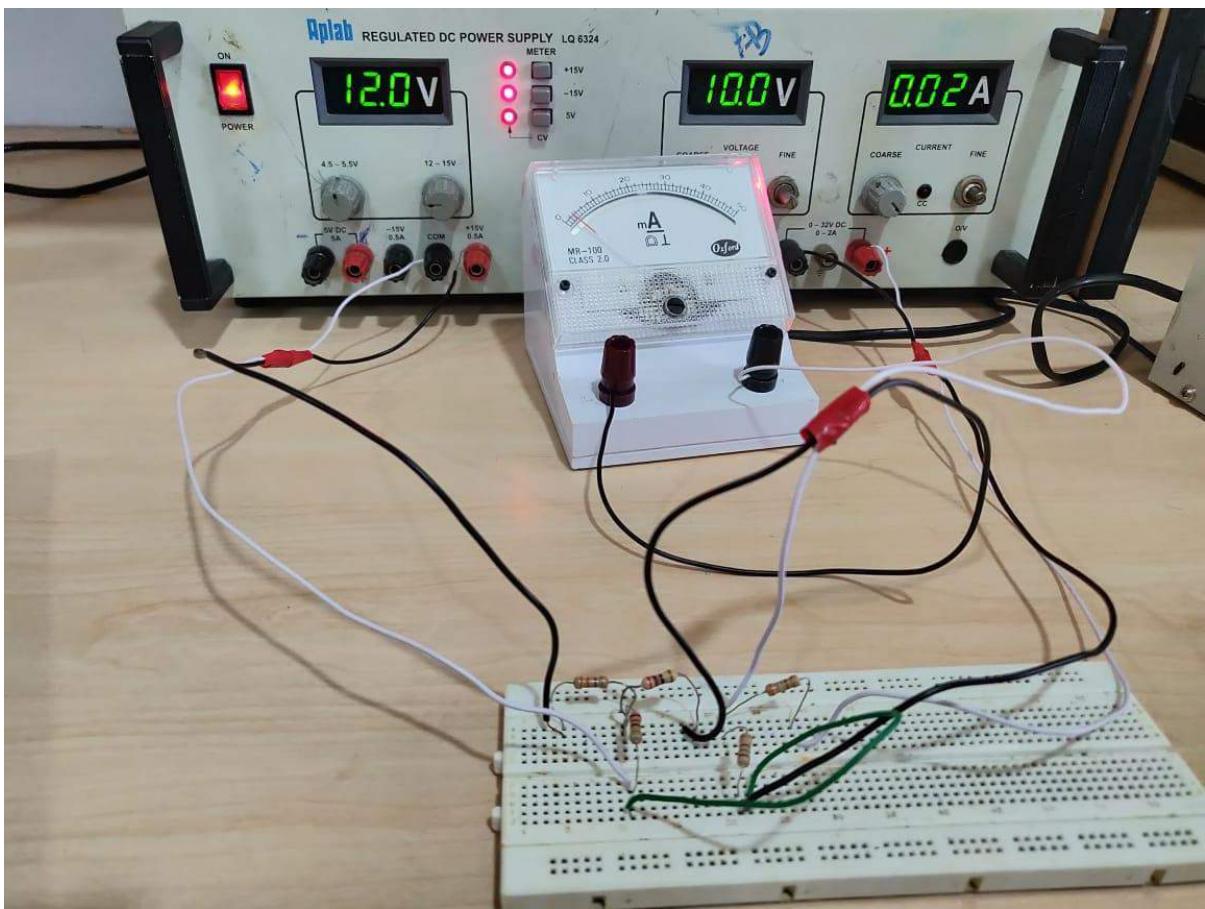

3. I3

