

## **LAB ASSIGNMENT – 8**

**Course:** Basic Electrical and Electronics Engineering

**Course Code:** EEE1001

**Faculty Name:** Prof. Medaramelta Praveenkumar

**Slot:** L-19+L-20

**Name:** Priyal Bhardwaj


**Registration Number:** 18BIT0272

**Submission Date:** 20.10.2018

## Verification of Thevenin's Theorem

**Aim:** Derive the Thevenin's equivalent circuit for the given circuit and verify it practically.

### Circuit Diagram

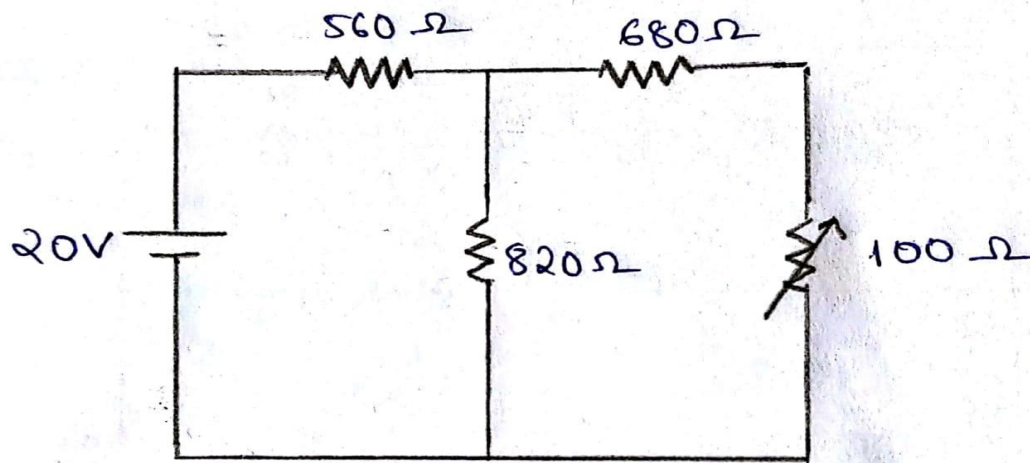

### Apparatus/Tool required:

Sl. No.	Components Name	Range	Quantity
1	Resister	120Ω, 330Ω, 470Ω, 220Ω, 100Ω	Each 1 No.
2	Ammeter	0-50mA (DC)	1 No.
3	Voltmeter	0-10V (DC)	1 No.
4	RPS	0-32 V (DC)	1 No.
5	Connecting Wires	-	Few
6	Bread Board	-	1 No.

### Theory

#### Statement: Thevenin's Theorem

Thevenin's Theorem states that "Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load."

It is possible to simplify any electrical circuit, no matter how complex.

Hardware Circuit:

To Find  $V_{TH}$ :

PHOTO OF CIRCUIT ATTACHED IN LAST PAGE

Reading:

Applied Voltage (Volts)	$V_{TH}$ (Volts)
20V	11.69V

To Find  $R_{TH}$ :

PHOTO OF CIRCUIT ATTACHED IN LAST PAGE

Reading:

Applied Voltage	Voltmeter Reading	Ammeter Reading	$R_{TH} = V/I$ ohms
10V	—	9 mA	1110
12V		11 mA	1090
14V		13 mA	1077

Average of  $R_{TH} = \underline{1093}$  Ohms.

To Find  $I_L$ :


PHOTO OF CIRCUIT ATTACHED IN LAST PAGE

Reading:

Applied Voltage (Volts)	Ammeter Reading (Amps)
11.6 V	11 mA

Manual Calculations:

To Find  $V_{th}$ :

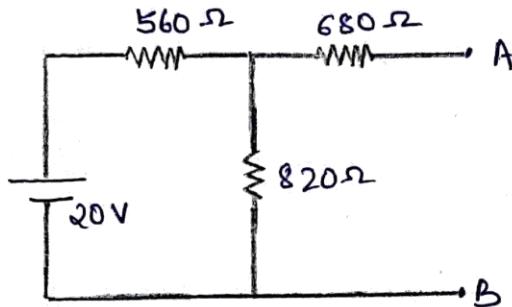


$$i = \frac{20}{(560 + 820)} = \frac{1}{69}$$

(current through 680 = 0)

$$V_{th} = i \times 820 = 11.88V$$


(voltage through 820 is  $V_{th}$  because 820 is in parallel)

To Find  $R_{th}$ :

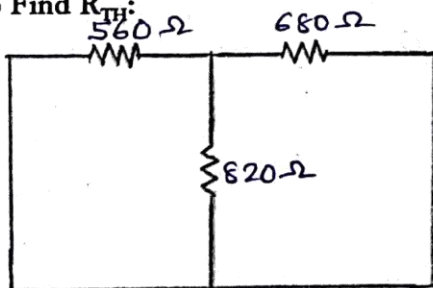


$$R_{th} = \frac{560 \times 820}{(560 + 820)} + 680$$

$$R_{th} = 1012.75 \Omega$$

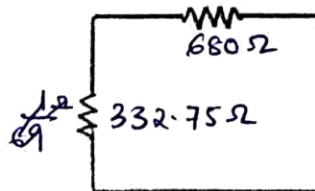

To Find  $I_L$ :

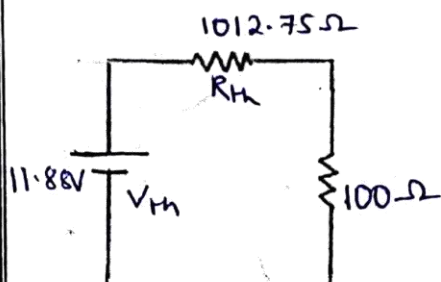

$$R = R_{th} + 100 = 1112.75 \Omega$$

$$V_{th} = IR \rightarrow I = \frac{V_{th}}{R}$$

$$I = \frac{11.88}{1112.75} = 10.67 \text{ mA}$$

**Procedure:**

- 1) Manually calculate,  $V_{th}$ ,  $R_{th}$  and  $I_L$  using Thevenin's Theorem.
- 2) For practical purpose connect the circuit as shown in the circuit diagrams.
- 3) First find current through the whole circuit.
- 4) To find  $V_{th}$ , remove ammeter,  $680\Omega$  resistor &  $100\Omega$  resistor and replace them with voltmeter.
- 5) To find  $R_{th}$ , remove voltmeter and reconnect  $680\Omega$  resistor, ammeter and connect a variable voltage source as shown in diagram.
- 6) Take 3 ammeter readings and calculate  $R_{th}$ .
- 7) Check if practical output is same as manual calculations.

**Result:**

**Thevenin's Theorem**

**Manual Calculations**

$$V_{th} = 11.88V$$

$$R_{th} = 1012.75\Omega$$

$$I_L = \frac{V_{th}}{R_{th}} = 11.7mA$$

$$I_L = 10.67mA$$

**Inference:**

**Practical Output**

$$V_{th} = 11.67V$$

$$R_{th} = 1093\Omega$$

$$I = 11mA$$


$$I_L = \frac{V_{th}}{R_{th}} = 10.67mA$$

Since manual calculations are same as practical output, Thevenin's Theorem is verified.


Reg. No: 18BIT0272 Name: PRIYAL BHARDWAJ Date: 20/10/2018





## MAIN CIRCUIT

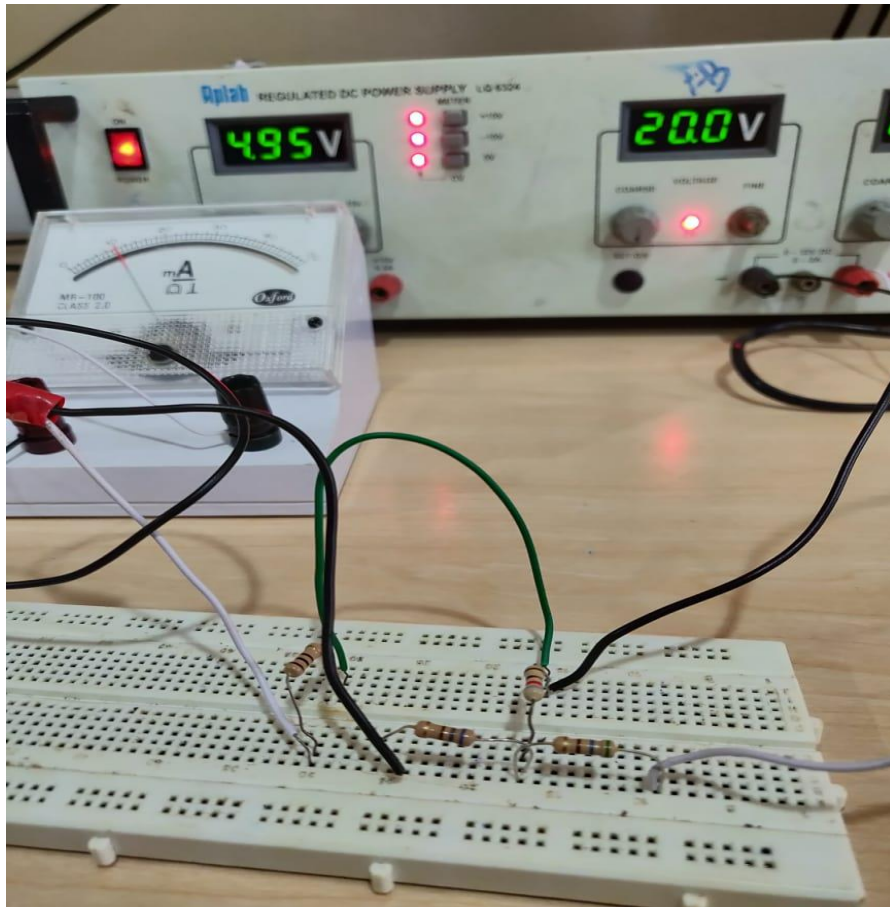


## TO FIND $V_{th}$ :

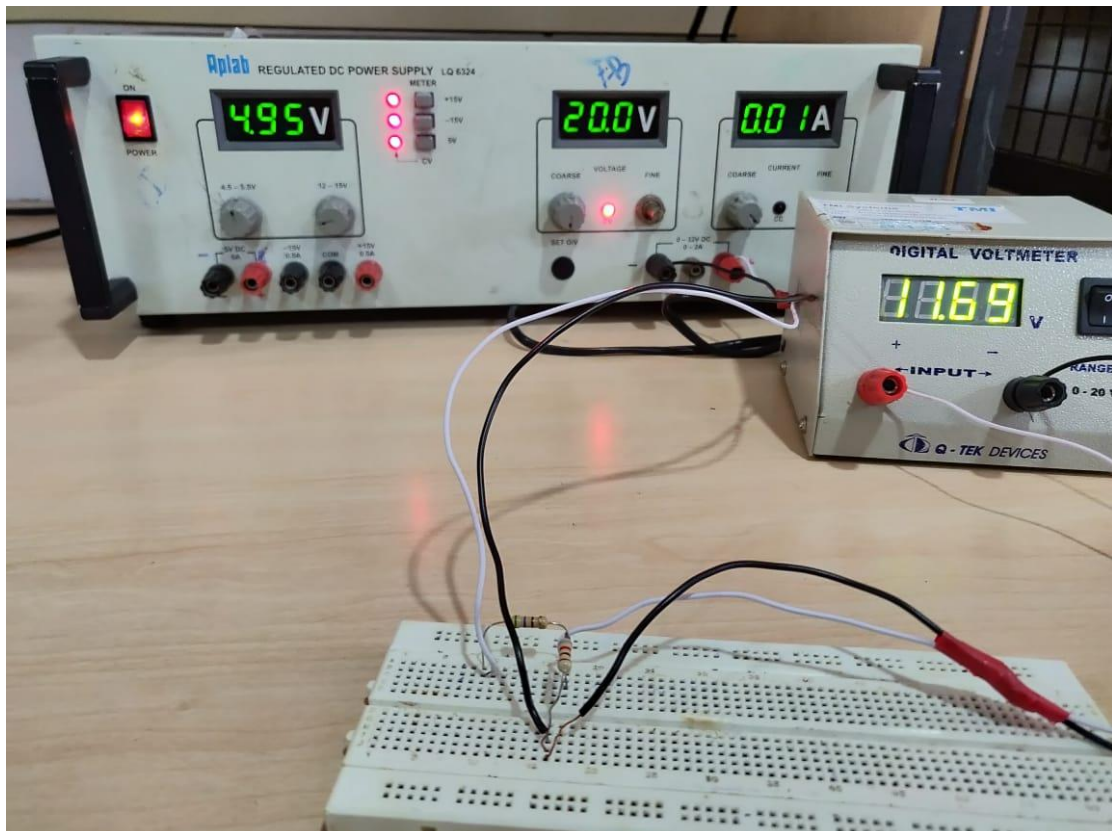

**TO FIND  $R_{th}$ :**

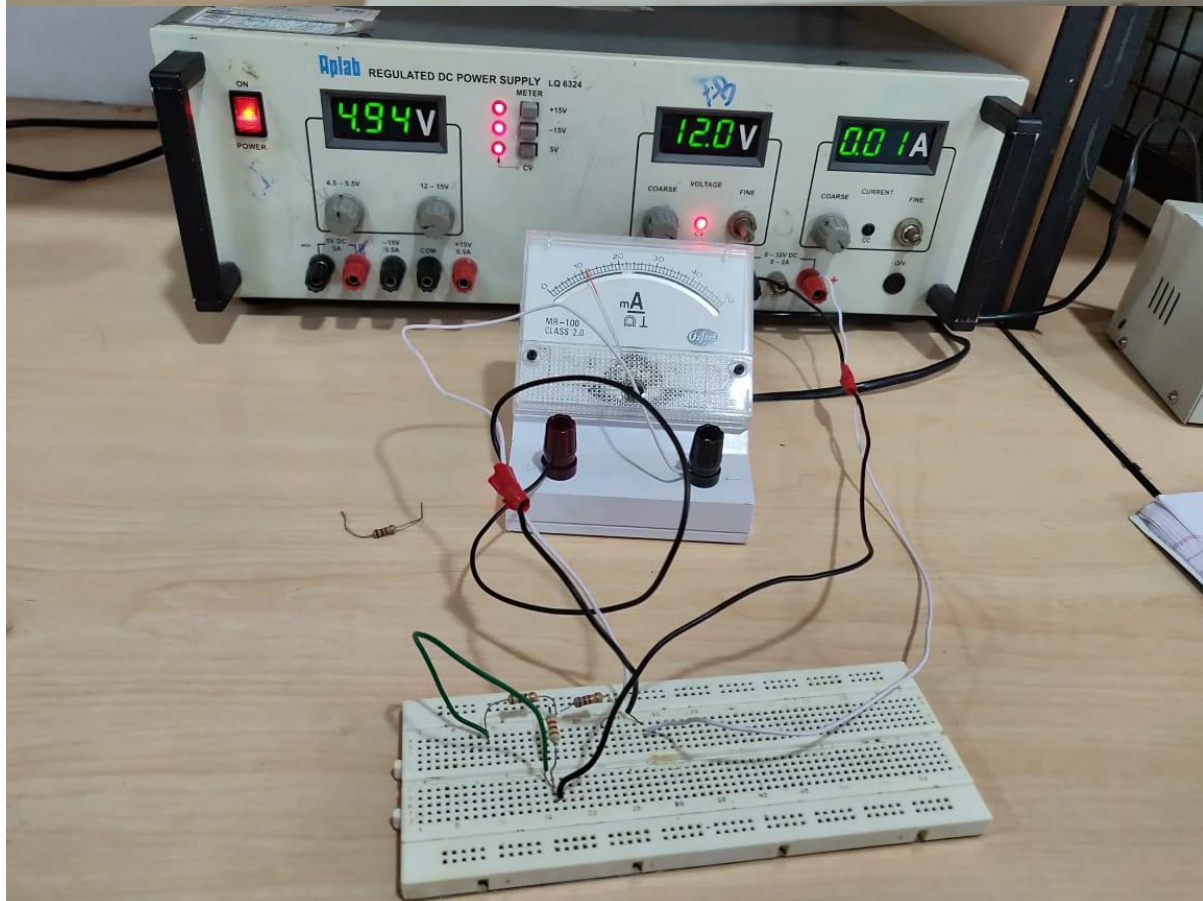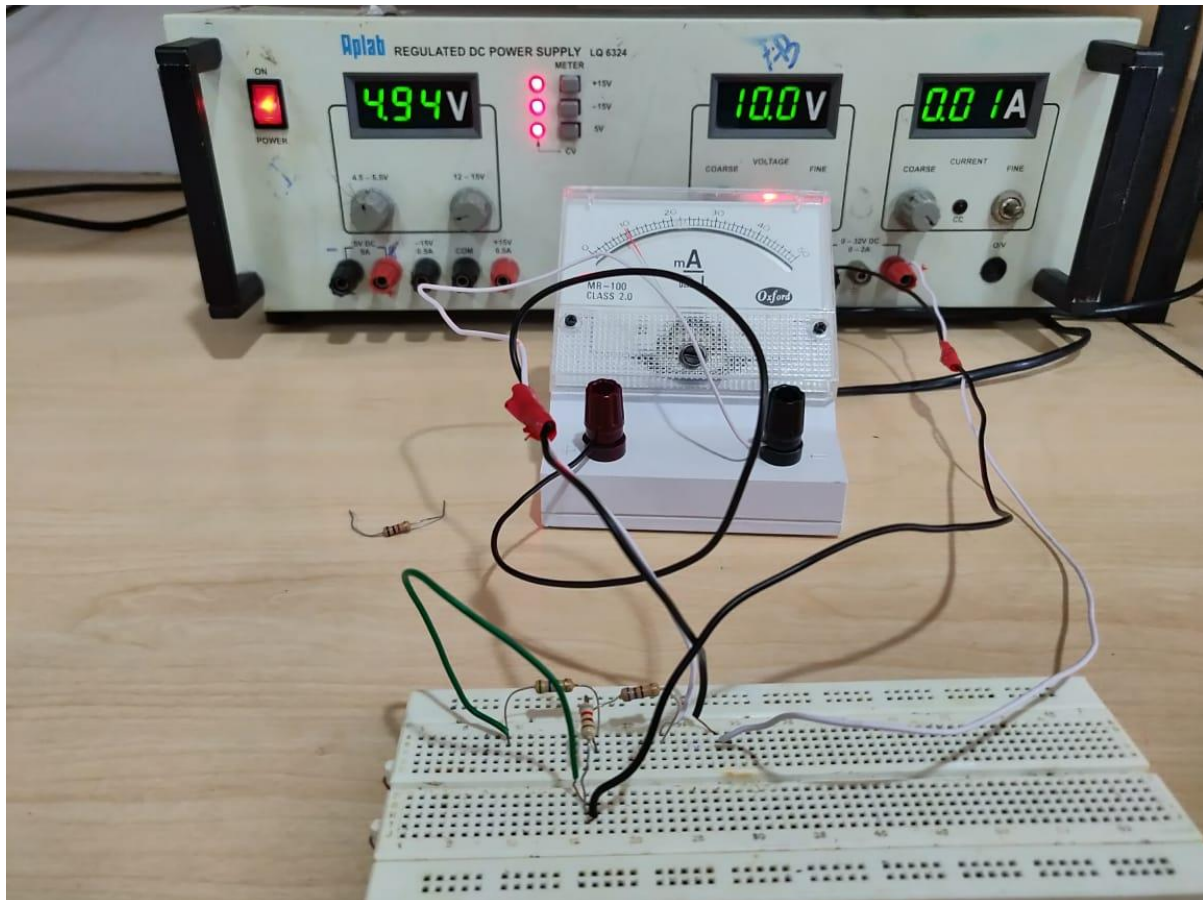




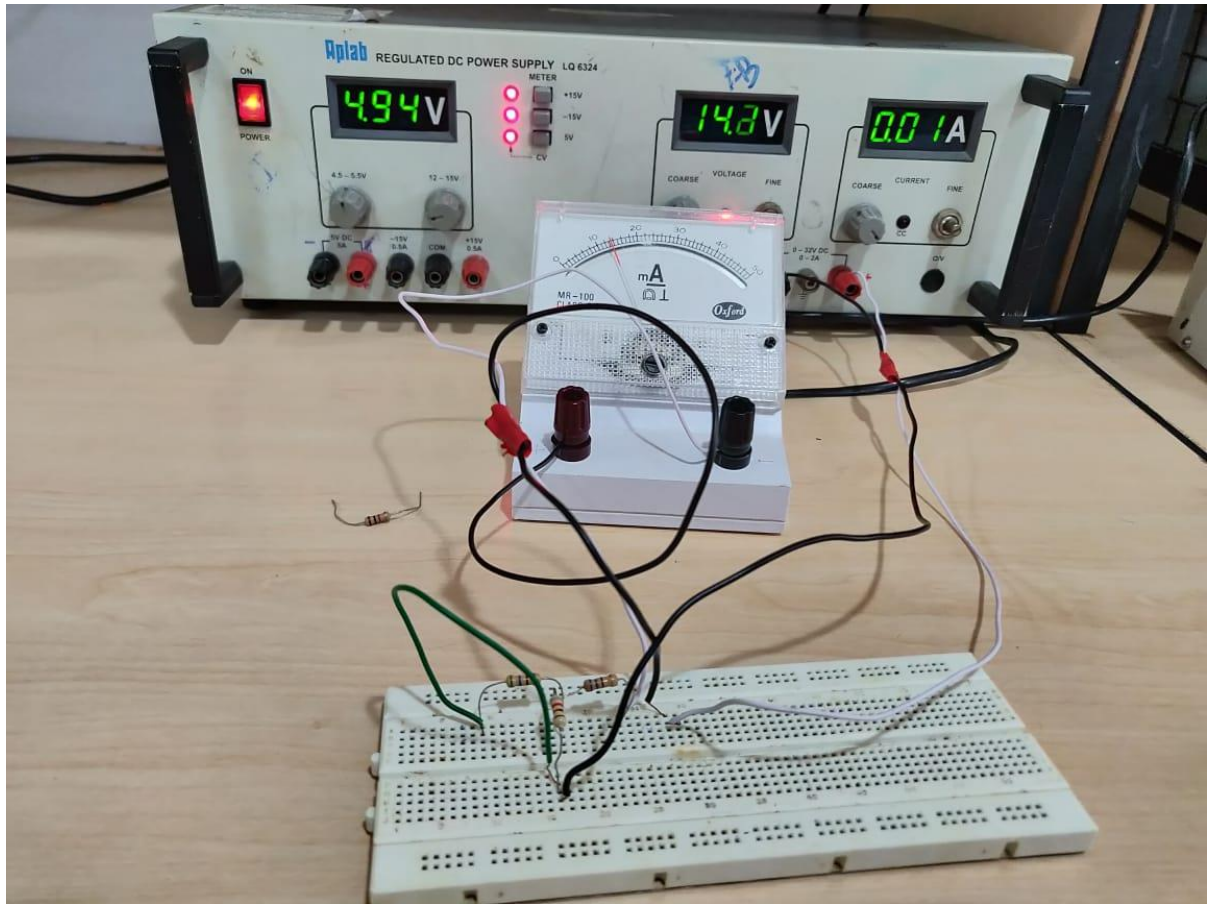


**TO FIND I:**

**1)  $I_1$**

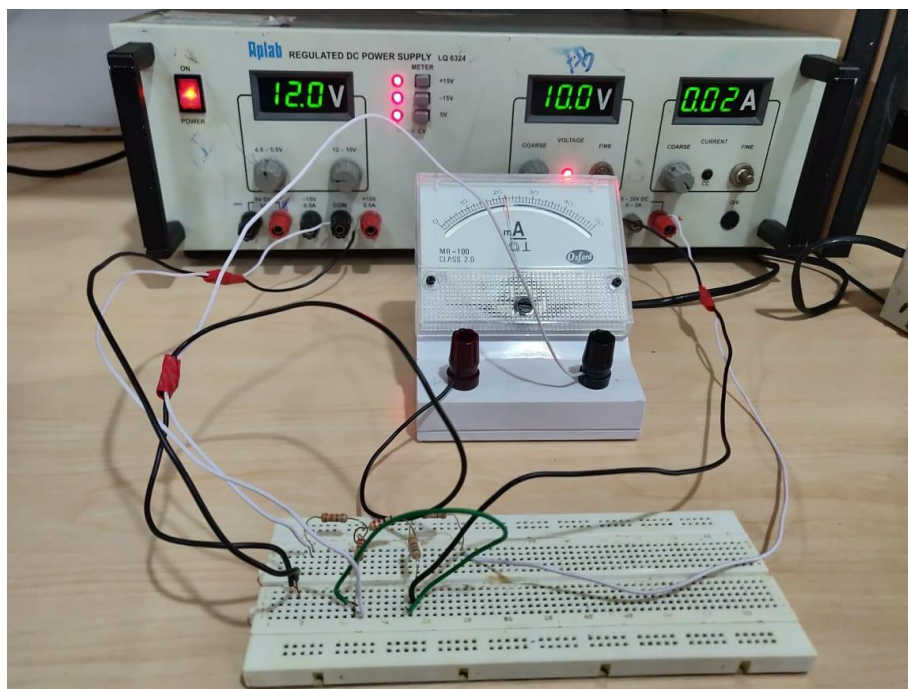



2) I<sub>2</sub>

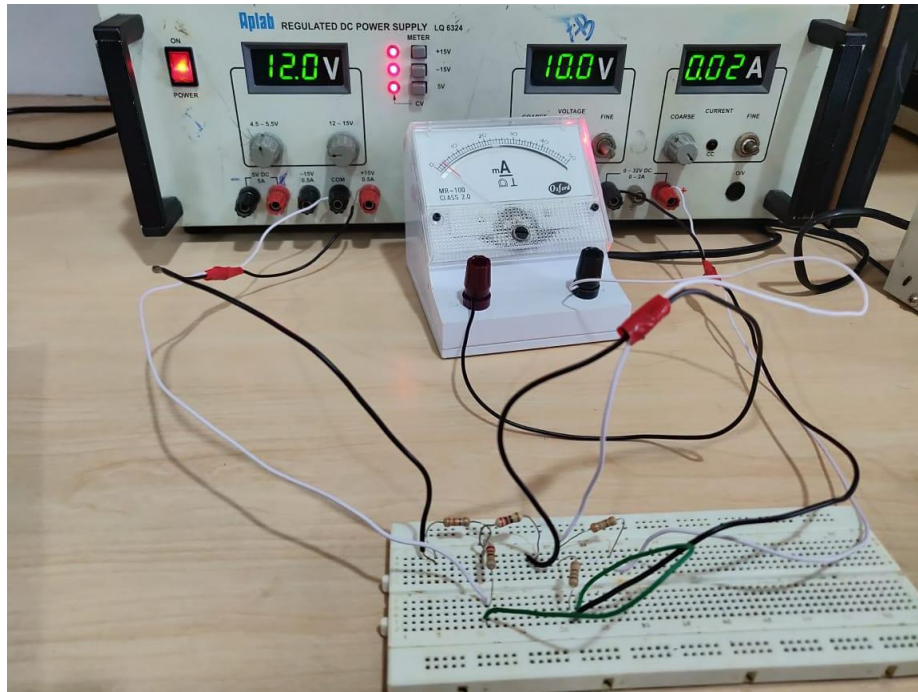

3) I<sub>3</sub>

