

DIGITAL LOGIC AND MICROPROCESSOR

Registration Number:	18BIT0272
Name:	PRIYAL BHARDWAJ
Slot:	L7+L8
Experiment Name:	Verification of GATES

OR GATE


Truth Table:

A	B	Output/C
0	0	0
0	1	1
1	0	1
1	1	1


Expression:

$$A+B=C$$


Multi Sim Circuit Diagram:

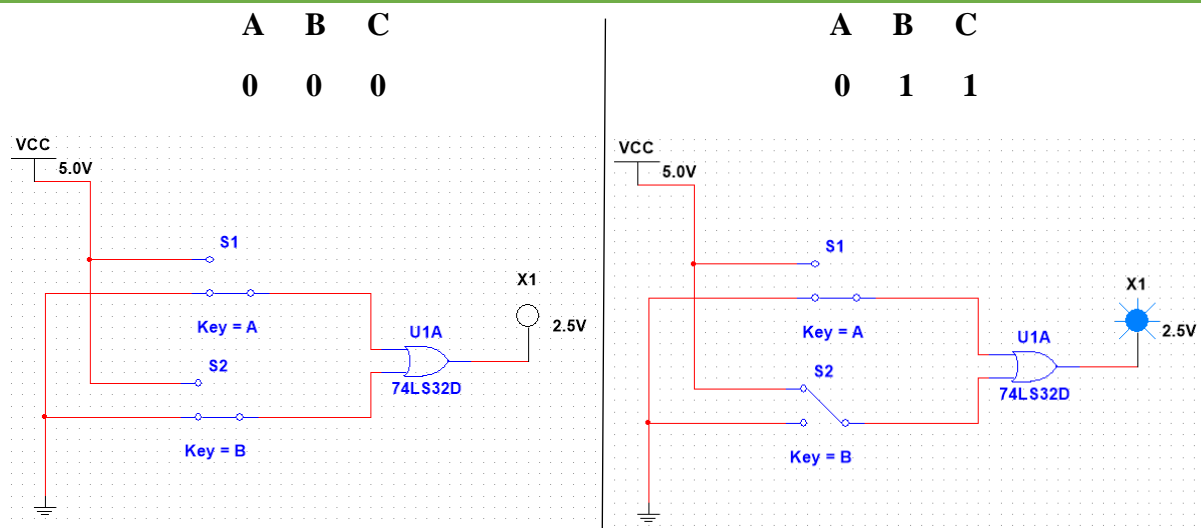

A B C
1 0 1

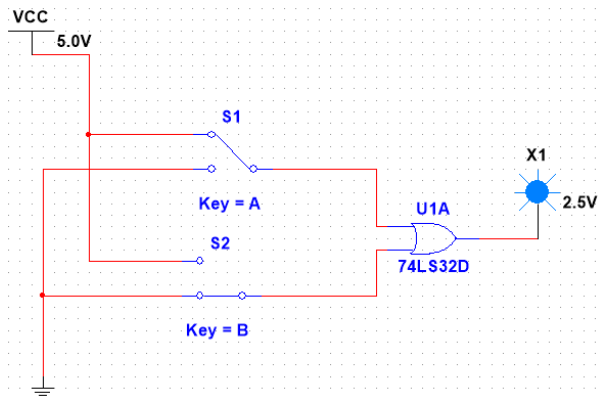

A B C
1 1 1

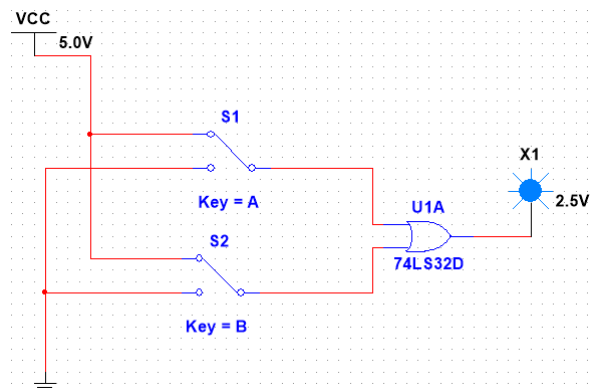

NOR GATE

Truth Table:


A	B	Output/C
0	0	1
0	1	0
1	0	0
1	1	0

Expression:


$$\overline{(A+B)}=C$$


Multi Sim Circuit Diagram:

A B C
0 0 1

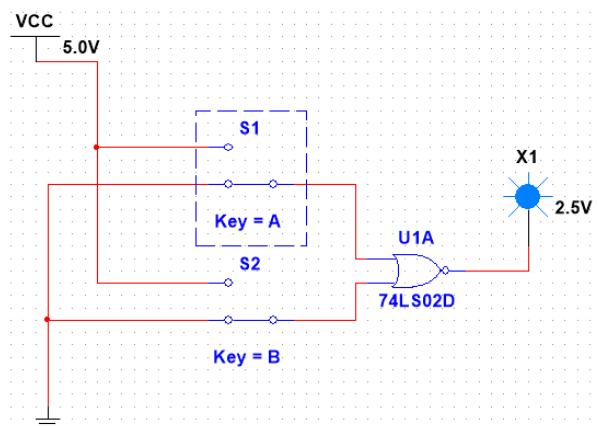

A B C
0 1 0

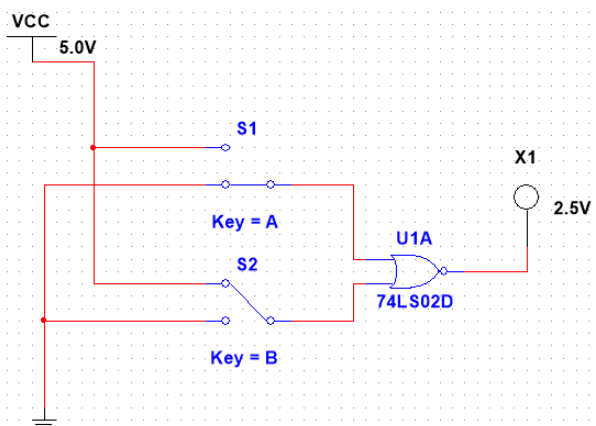

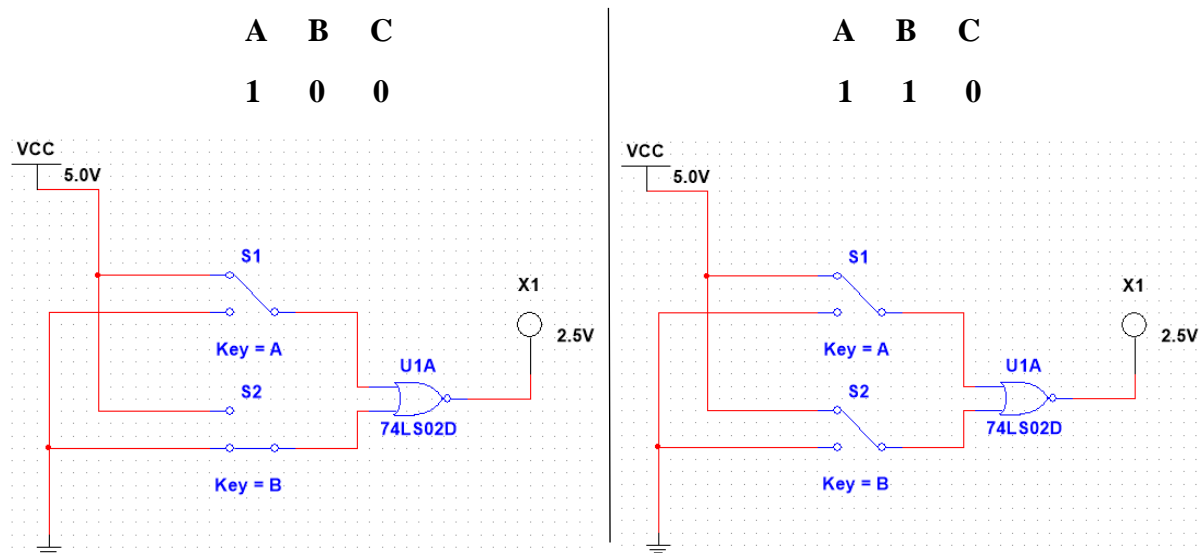

AND GATE


Truth Table:


A	B	Output/C
0	0	0
0	1	0
1	0	0
1	1	1

Expression:

$$AB=C$$

Multi Sim Circuit Diagram:

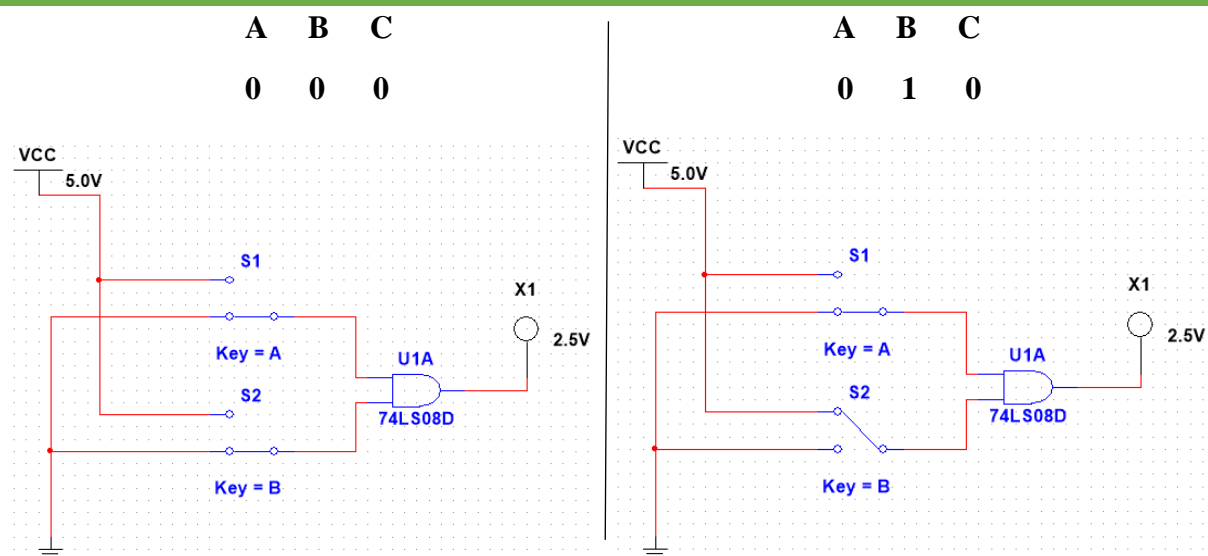

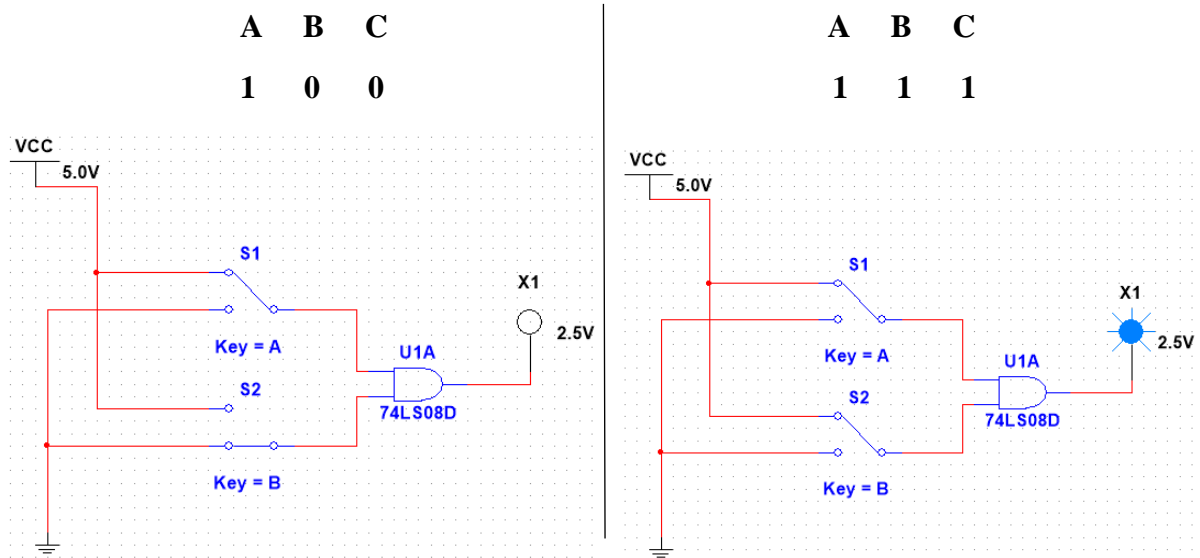

NAND GATE


Truth Table:


A	B	Output/C
0	0	1
0	1	1
1	0	1
1	1	0

Expression:

$$\overline{A}\overline{B}=C$$

Multi Sim Circuit Diagram:

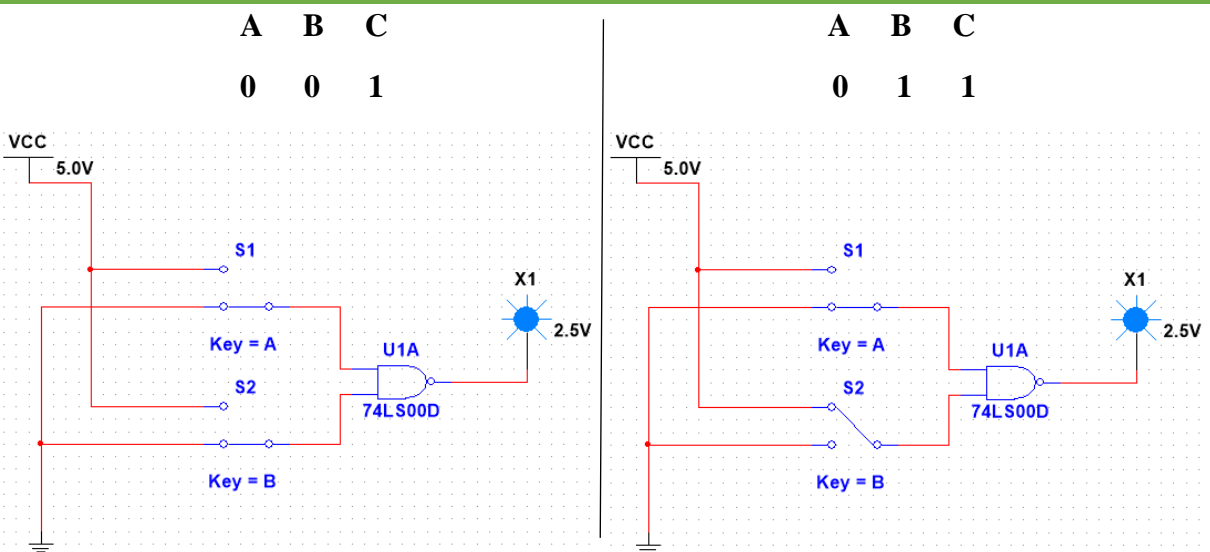

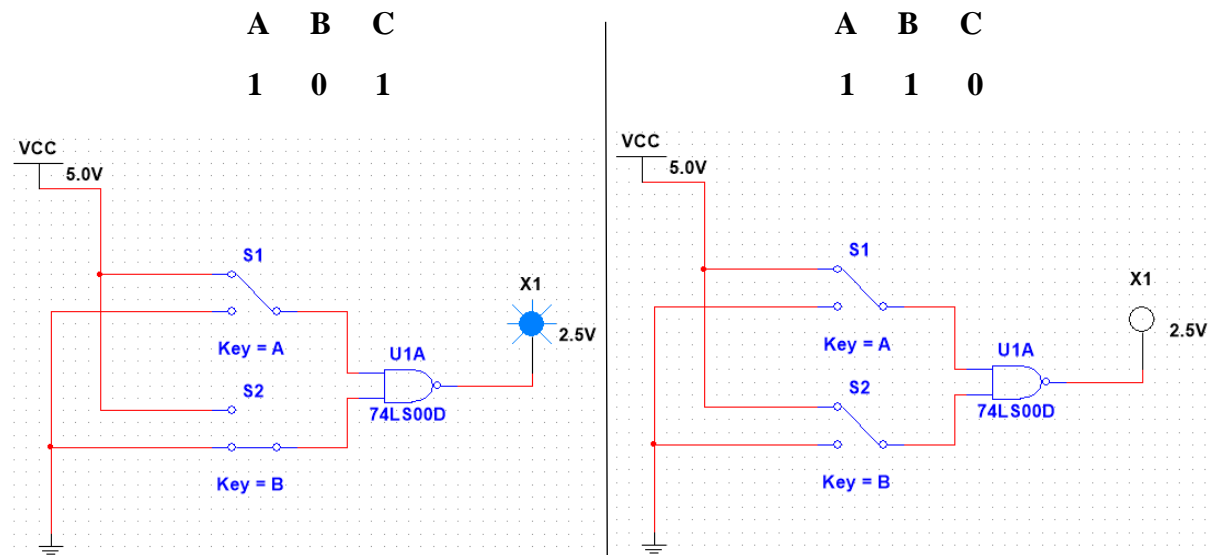

NOT GATE


Truth Table:

A	\overline{A}
0	1
1	0

Expression:

$$A = \overline{A}$$

Multi Sim Circuit Diagram:

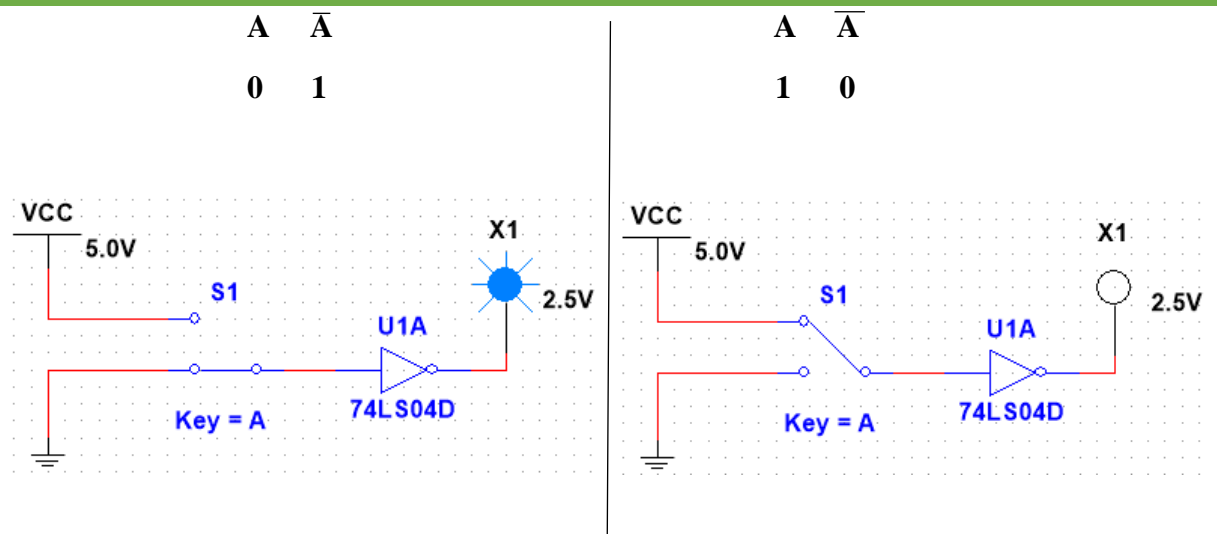

XOR GATE


Truth Table:

A	B	Output/C
0	0	0
0	1	1
1	0	1
1	1	0

Expression:

$$\overline{A}B + A\overline{B} = C$$

Multi Sim Circuit Diagram:

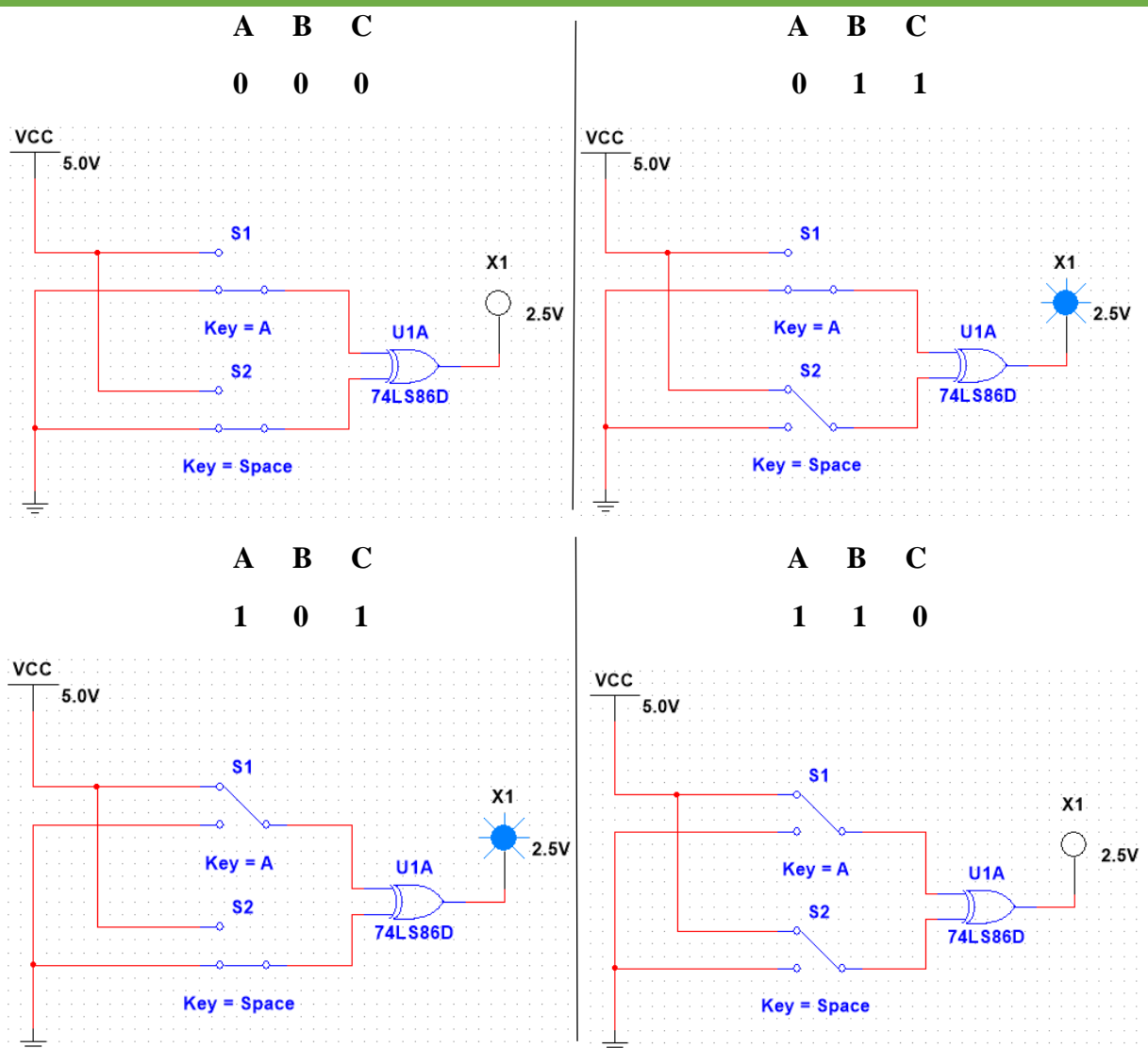

XNOR GATE


Truth Table:

A	B	Output/C
0	0	1
0	1	0
1	0	0
1	1	1


Expression:

$$AB + \overline{A}\overline{B} = C$$


Multi Sim Circuit Diagram:

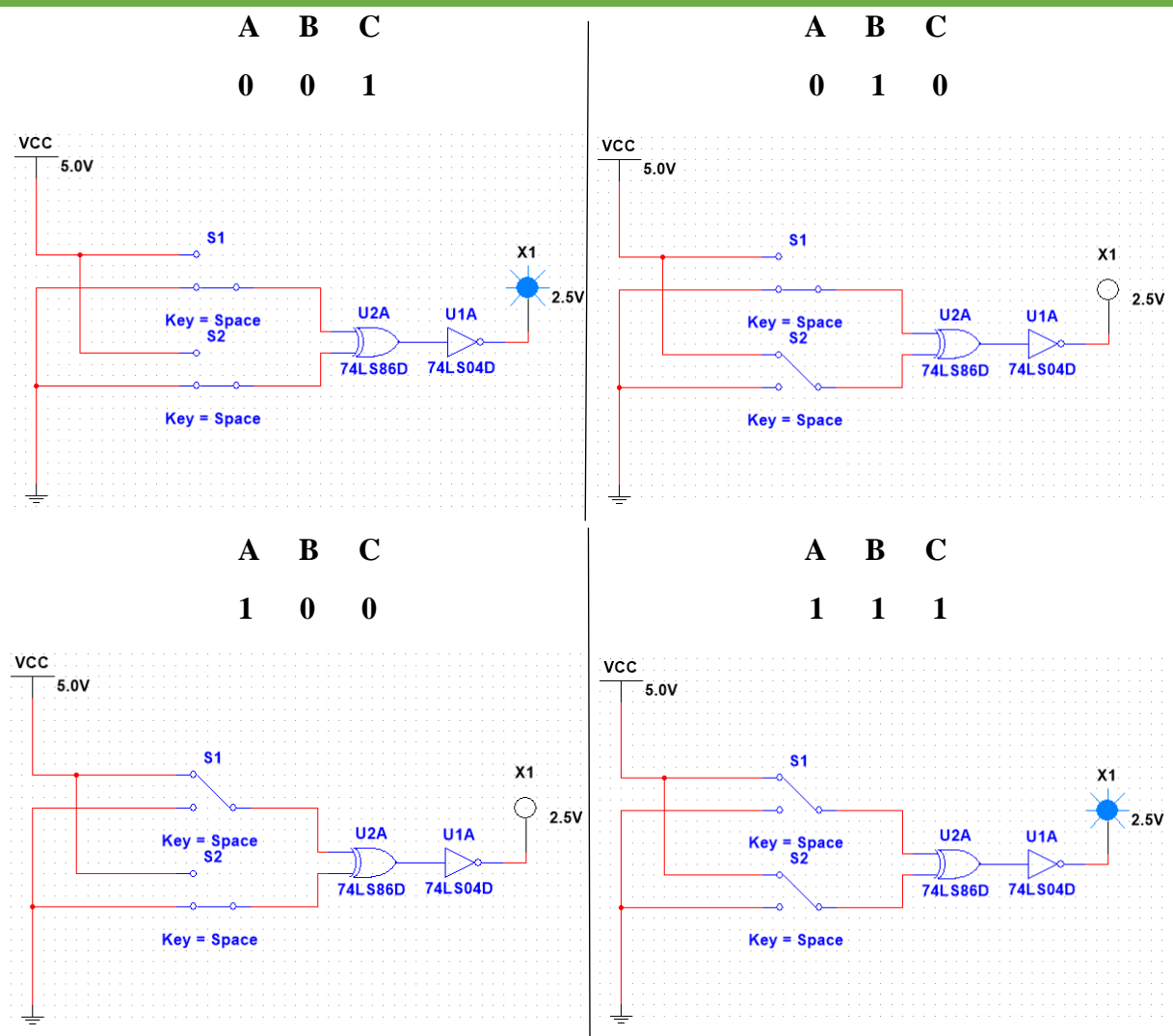


OR GATE:

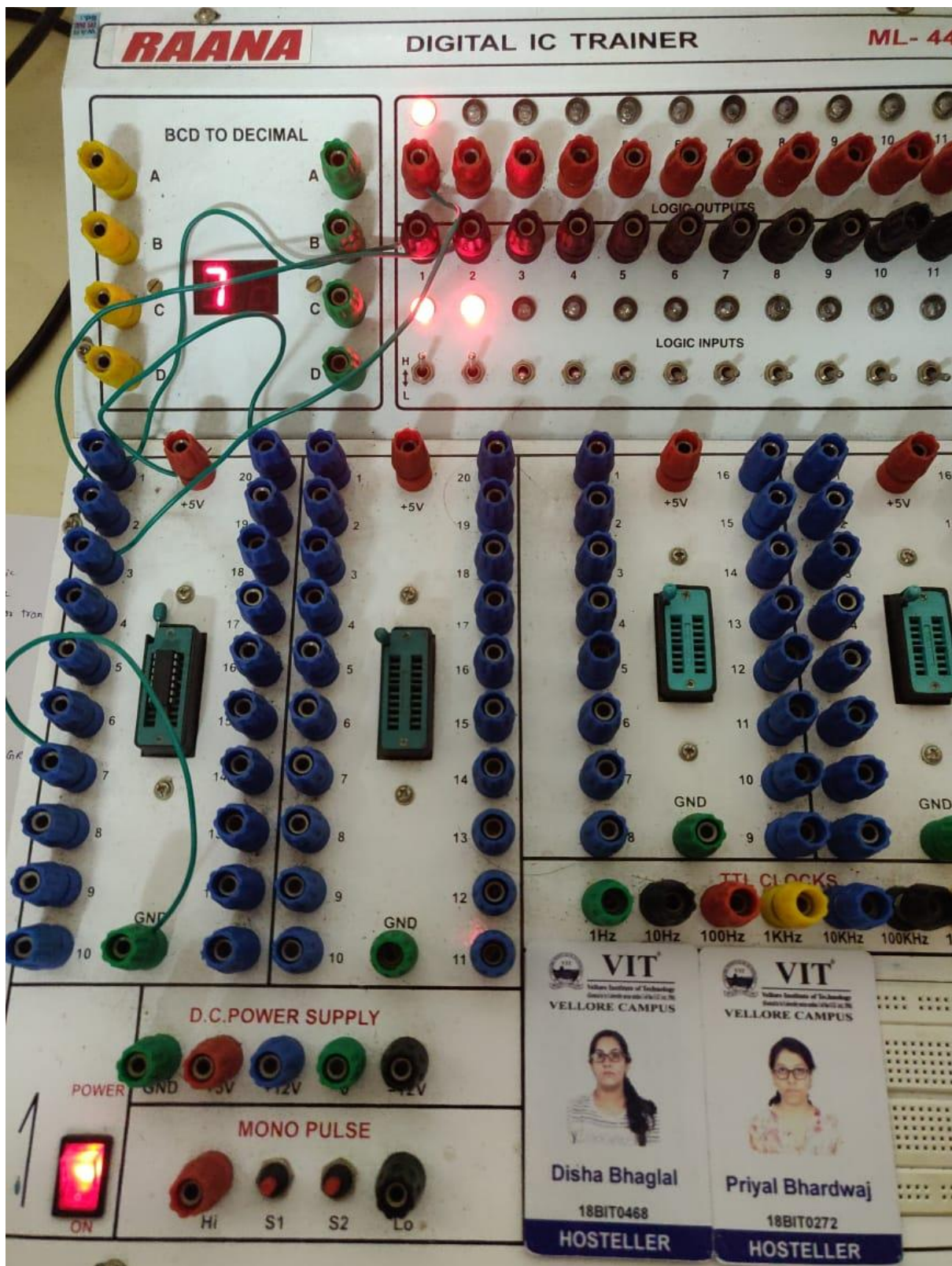


NAND GATE:

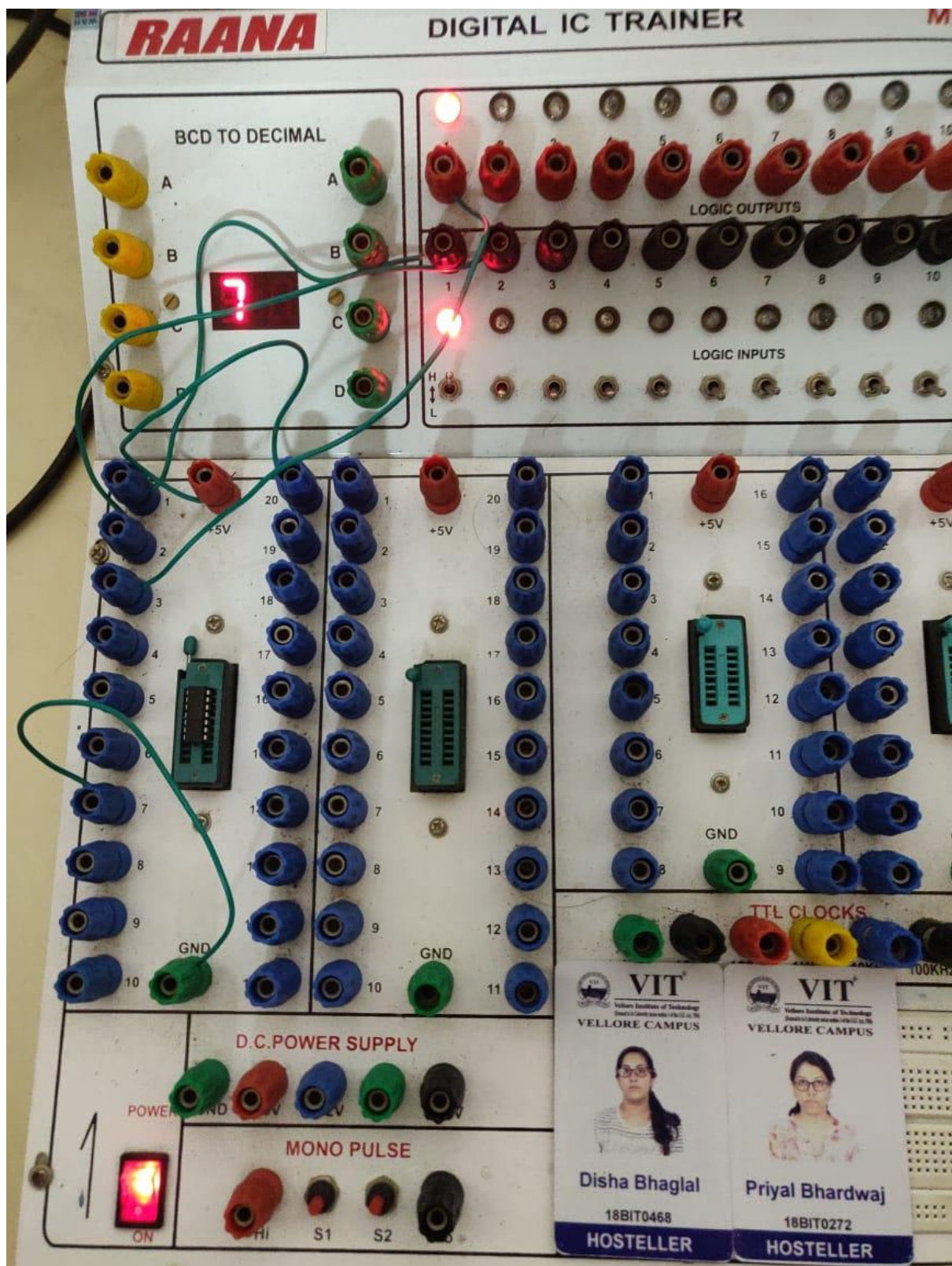

EX-OR GATE:

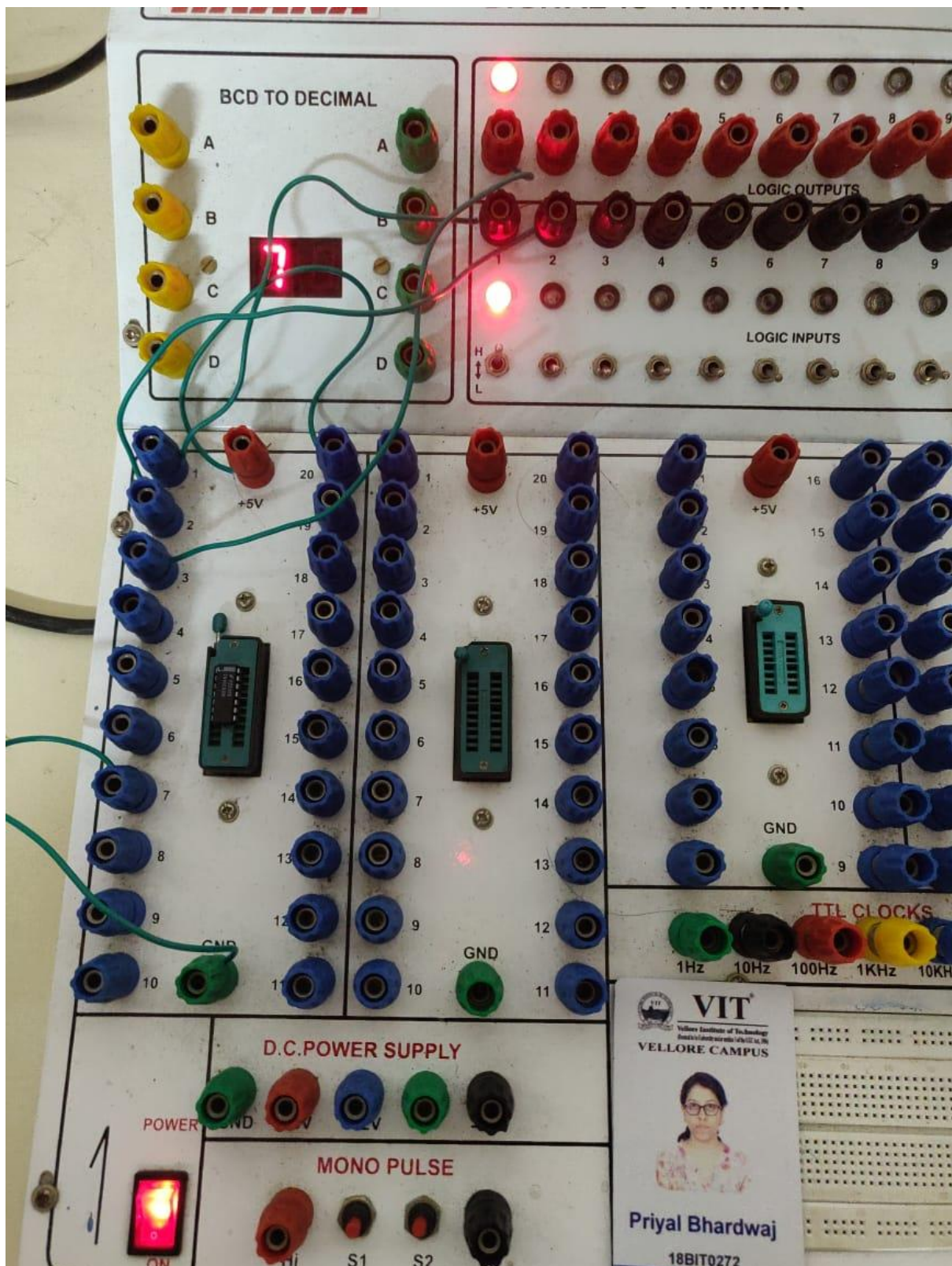

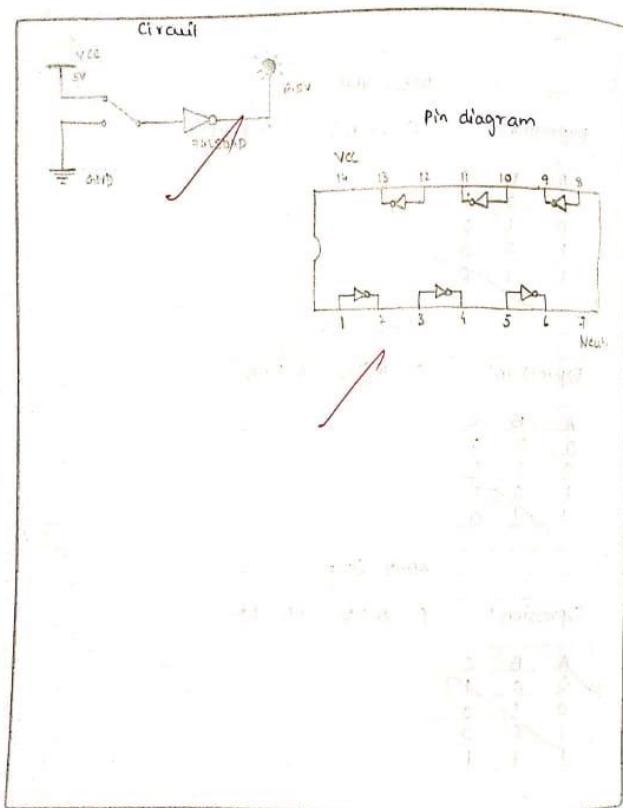

Expt. No. Date

Page No. ... 3 ...

NOT GATE

Expression :- $B = \bar{A}$

A	B
0	1
1	0

H/w completed
M. Ghuman

Teacher's Signature :

Experiment Name: Implementation of Boolean Expressions


1. Implement the following Boolean Expressions using Basic Logic Gates

a. $F = AB + C'D$


Truth Table:

A	B	C	D	C'	AB	C'D	F
0	0	0	0	1	0	0	0
0	0	0	1	1	0	1	1
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	1	1
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	1
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	1


Multi Sim Circuit Diagram:

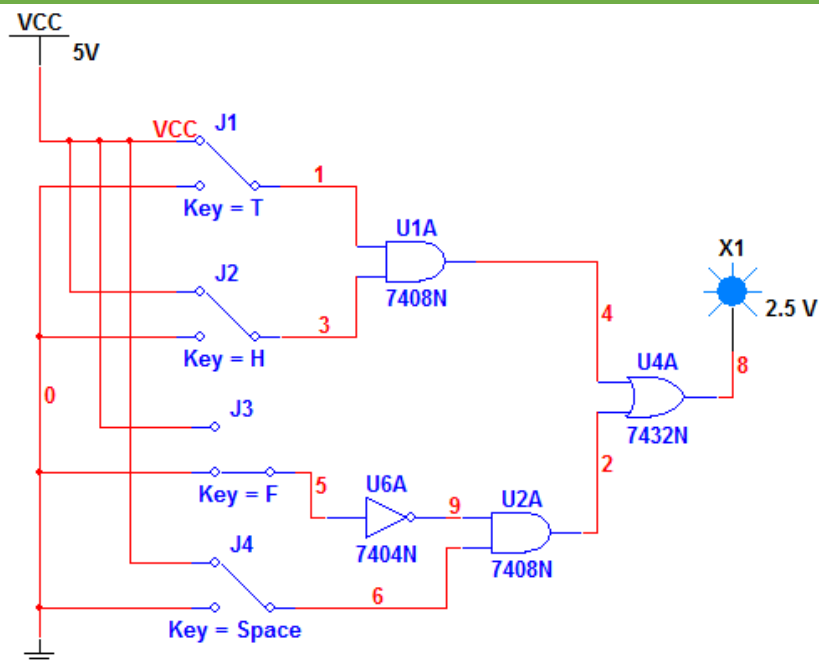

HARDWARE:

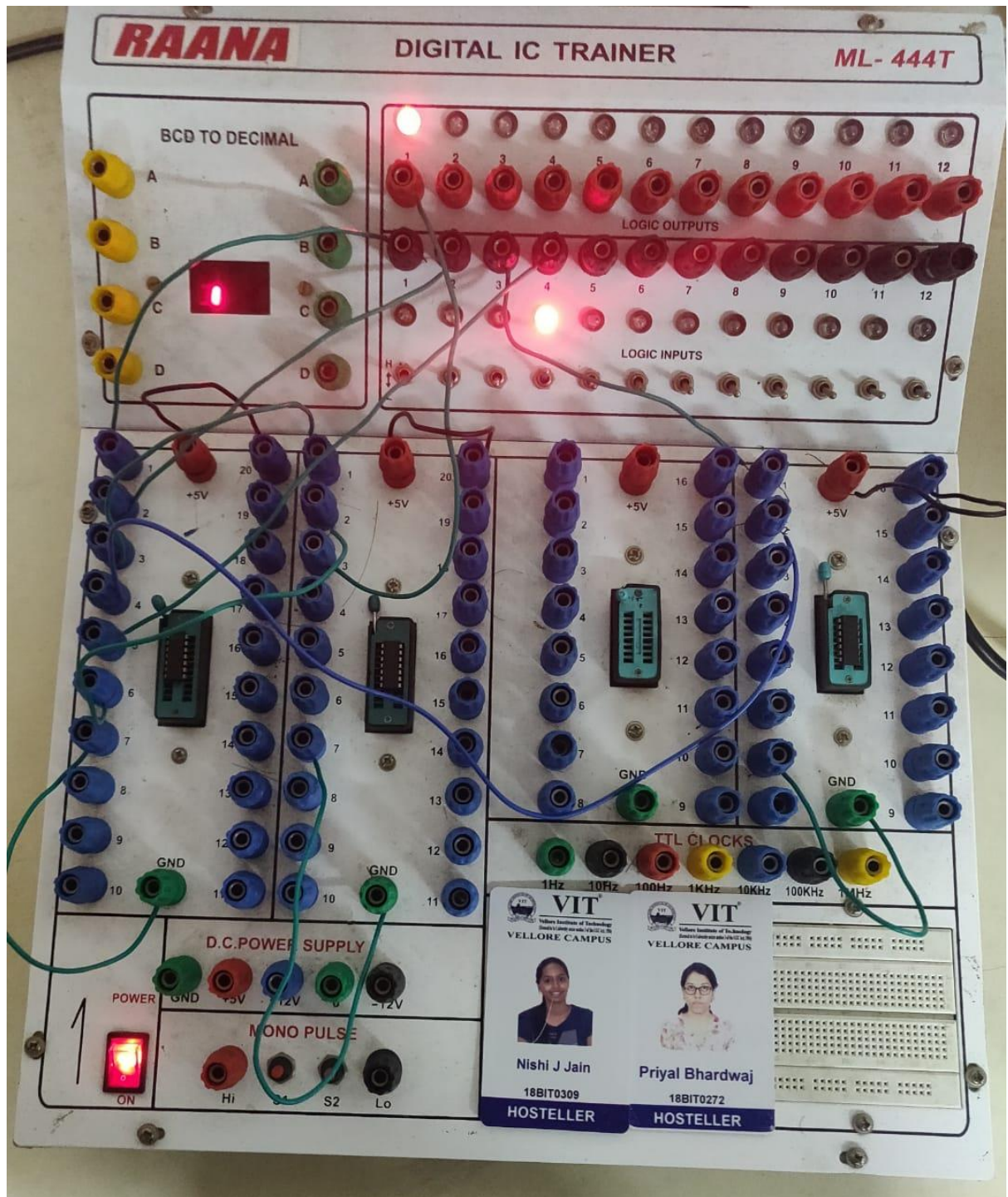

4(a)

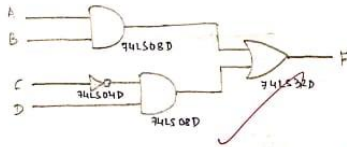

*H/w verified
M. S. P.*

Expt. No. 2

Date
Page No. 4

Implementation of Boolean expressions

(1) Implement the following boolean expressions using logic gates

(a) $F = AB + \bar{C}D$

A	B	C	D	\bar{C}	AB	$\bar{C}D$	F
0	0	0	0	1	0	0	0
0	0	0	1	1	0	1	1
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	1	1
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	1
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	1

Teacher's Signature : _____


b. $F = ABC' + DE'F$

Truth Table:

A	B	C	D	E	F	C'	E'	ABC'	DE'F	F
0	0	0	0	0	0	1	1	0	0	0
0	0	0	0	0	1	1	1	0	0	0
0	0	0	0	1	0	1	0	0	0	0
0	0	0	0	1	1	1	0	0	0	0
0	0	0	1	0	0	1	1	0	0	0
0	0	0	1	0	1	1	1	0	1	1
0	0	0	1	1	0	1	0	0	0	0
0	0	0	1	1	1	1	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0
0	0	1	0	0	1	0	1	0	0	1
0	0	1	0	1	0	0	0	0	0	0
0	0	1	0	1	1	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0
0	0	1	1	0	1	0	1	0	1	1
0	0	1	1	1	0	0	0	0	0	0
0	0	1	1	1	1	0	0	0	0	0
0	1	0	0	0	0	1	1	0	0	0
0	1	0	0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	1	0	0	0	0
0	1	0	1	0	0	1	1	0	0	0
0	1	0	1	0	1	1	1	0	1	1
0	1	0	1	1	0	1	0	0	0	0
0	1	0	1	1	1	1	0	0	0	0
0	1	1	0	0	0	0	1	0	0	0
0	1	1	0	0	1	0	1	0	0	0
0	1	1	0	1	0	0	0	0	0	0
0	1	1	0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	1	0	0	0
0	1	1	1	0	1	0	1	0	1	1
0	1	1	1	1	0	0	0	0	0	0
0	1	1	1	1	1	0	0	0	0	0
1	0	0	0	0	0	1	1	0	0	0
1	0	0	0	0	1	1	1	0	0	0
1	0	0	0	1	0	1	0	0	0	0
1	0	0	0	1	1	1	0	0	0	0
1	0	0	1	0	0	1	1	0	0	0
1	0	0	1	0	1	1	1	0	1	1
1	0	0	1	1	0	1	0	0	0	0
1	0	0	1	1	1	1	0	0	0	0
1	0	1	0	0	0	0	1	0	0	0
1	0	1	0	0	1	0	1	0	0	0

1	0	1	0	1	0	0	0	0	0	0
1	0	1	0	1	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0
1	0	1	1	0	1	0	1	0	1	1
1	0	1	1	1	0	0	0	0	0	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	0	0	1	1	1	0	0
1	1	0	0	0	1	1	1	1	0	0
1	1	0	0	1	0	1	0	1	0	0
1	1	0	0	1	1	1	0	1	0	0
1	1	0	1	0	0	1	1	1	0	0
1	1	0	1	0	1	1	1	1	1	1
1	1	0	1	1	0	1	0	1	0	0
1	1	0	1	1	1	1	0	1	0	0
1	1	1	0	0	0	0	1	0	0	0
1	1	1	0	0	1	0	1	0	0	0
1	1	1	0	1	0	0	0	0	0	0
1	1	1	0	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1	0	0	0
1	1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	0	0	0	0	0	0
1	1	1	1	1	1	0	0	0	0	0

Multi Sim Circuit Diagram:

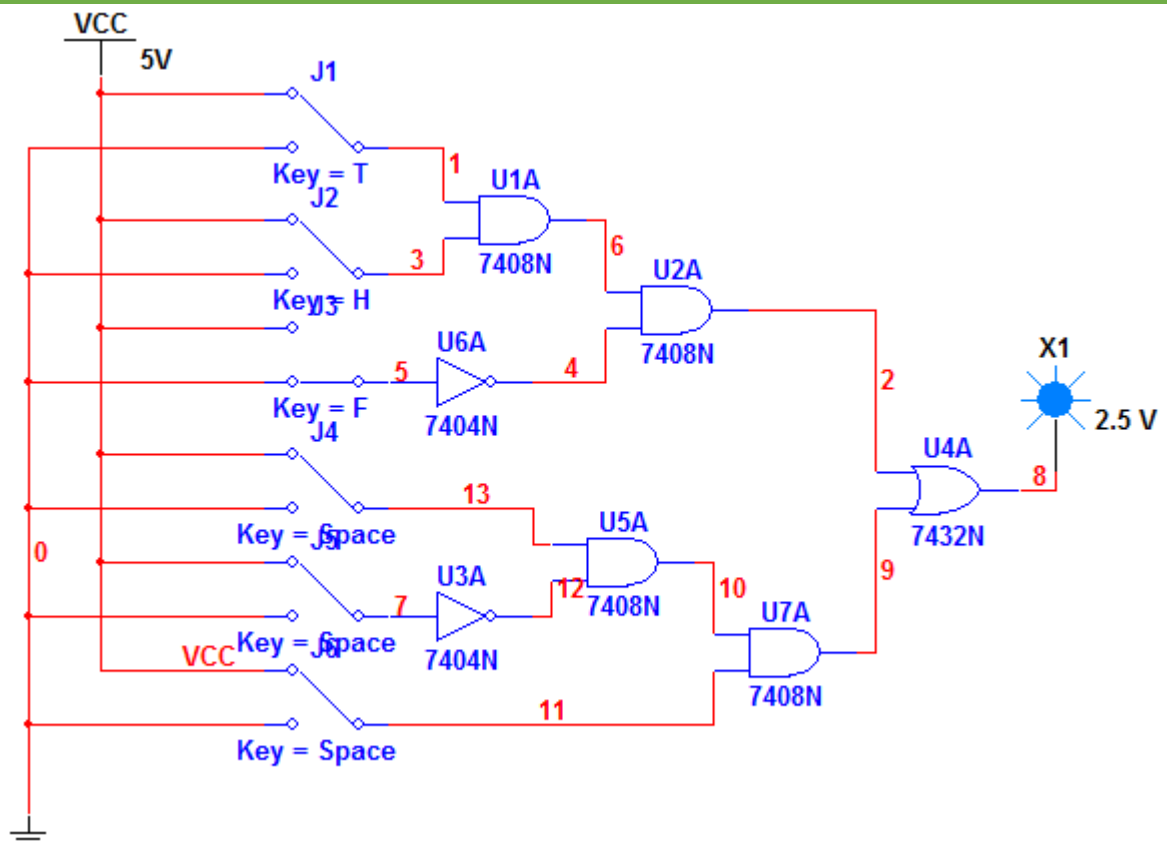


2. Implement the NAND Equivalent circuit for the Boolean Expression

i. $F = AB + BC' + C'$

Truth Table:

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Multi Sim Circuit Diagram:

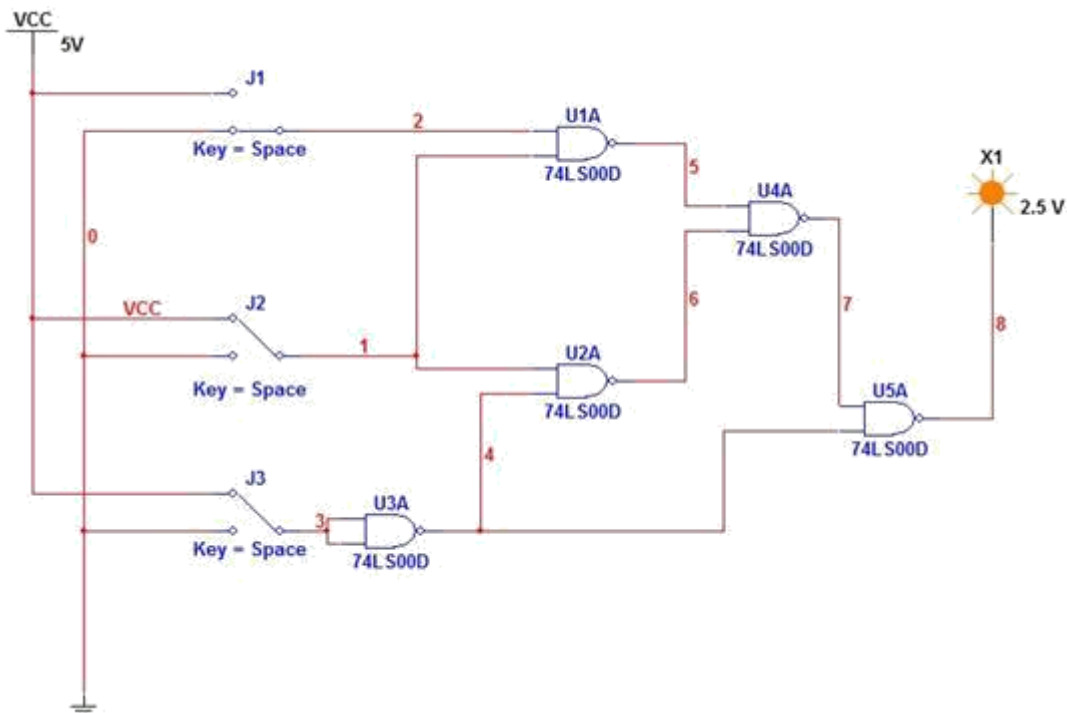


ii. $F = (ABC)(A+B+C)$

Truth Table:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Multi Sim Circuit Diagram:

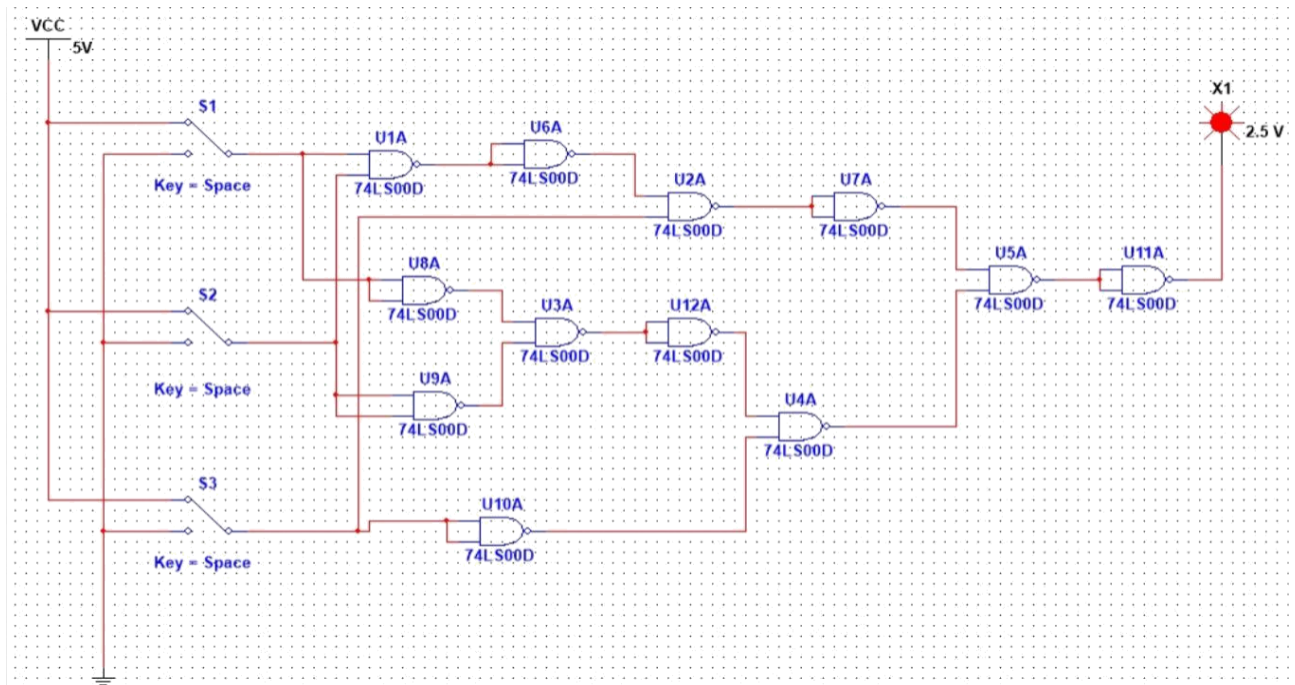


iii. $F = (A' + B' + C')(A'B')$

Truth Table:

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Multi Sim Circuit Diagram:

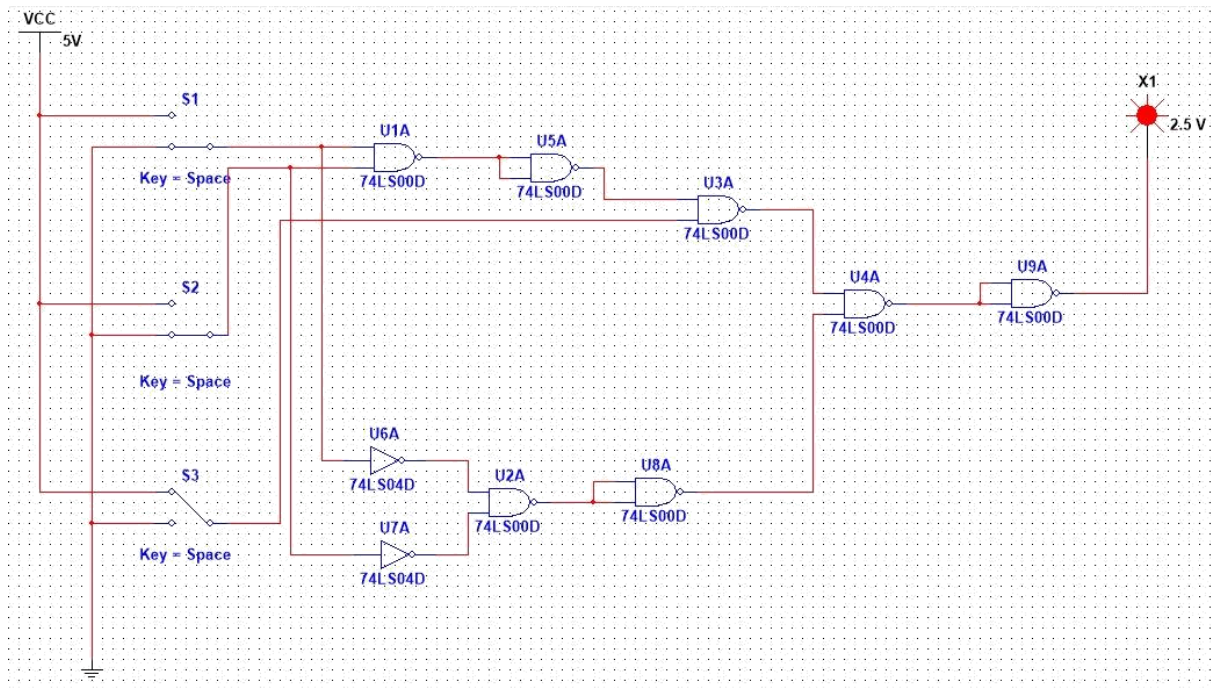

Experiment Name: Design of Combinational Circuits

1. A manufacturing plant needs to have a horn sound to signal quitting time. The horn should be activated when either of the following conditions is met:

- a. It's after 5 o'clock and all machines are shut down.
- b. Its Friday, the production run for the day is complete, and all machines are shut down.

Design a logic circuit that will control the horn. (Hint: use four logic input variables to represent the various conditions, for example, input A will be High only when the time of day is 5 o'clock or later).

Truth Table:


A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Expression:

$$F(A,B,C,D)=m(7,12,13,14,15)$$

$$F=AB+BCD$$

Multi Sim Circuit Diagram:

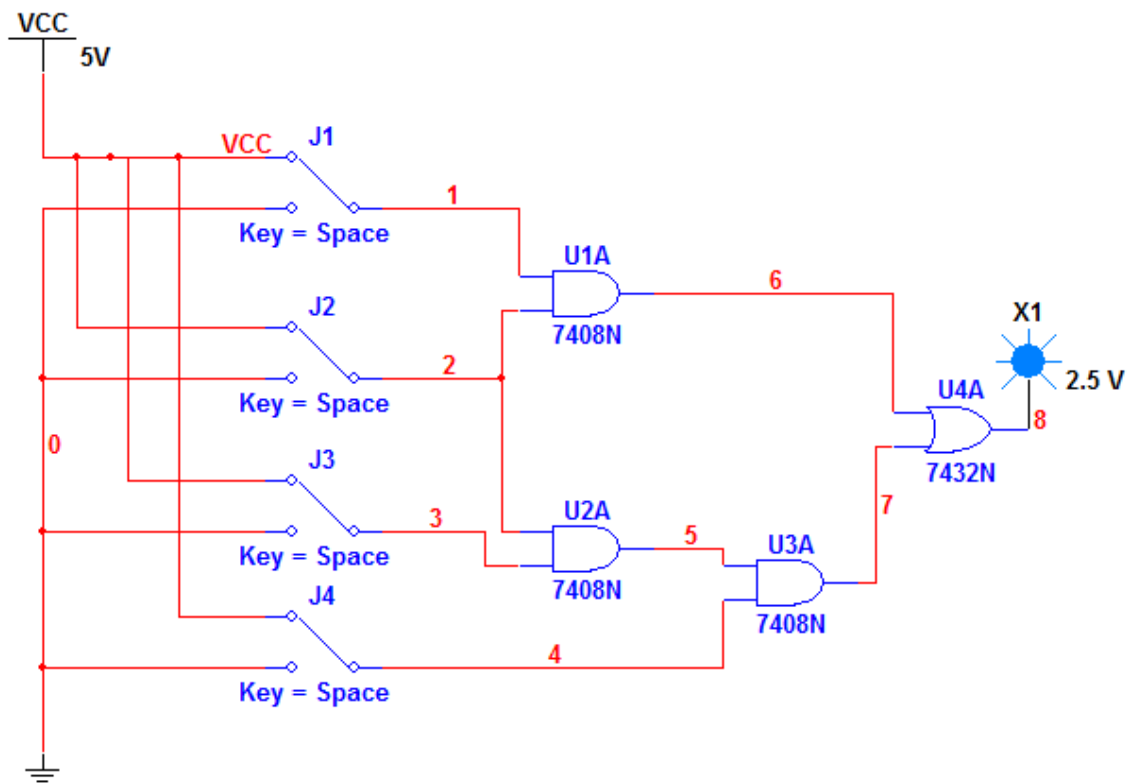

2. A bank vault has three locks with a different key for each lock. Each key is owned by a different person. In order to open the door, at least two people must insert their keys into the assigned locks. The signals A, B, and C are 1 if there is a key inserted into lock 1, 2, or 3, respectively. Write an equation for the variable Z, which is 1 if the door should open. Implement the same using basic gates.

Truth Table:


A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Expression:

$$Z(A,B,C)=m(3,5,6,7)$$

$$Z=AB+BC+AC$$

Multi Sim Circuit Diagram:

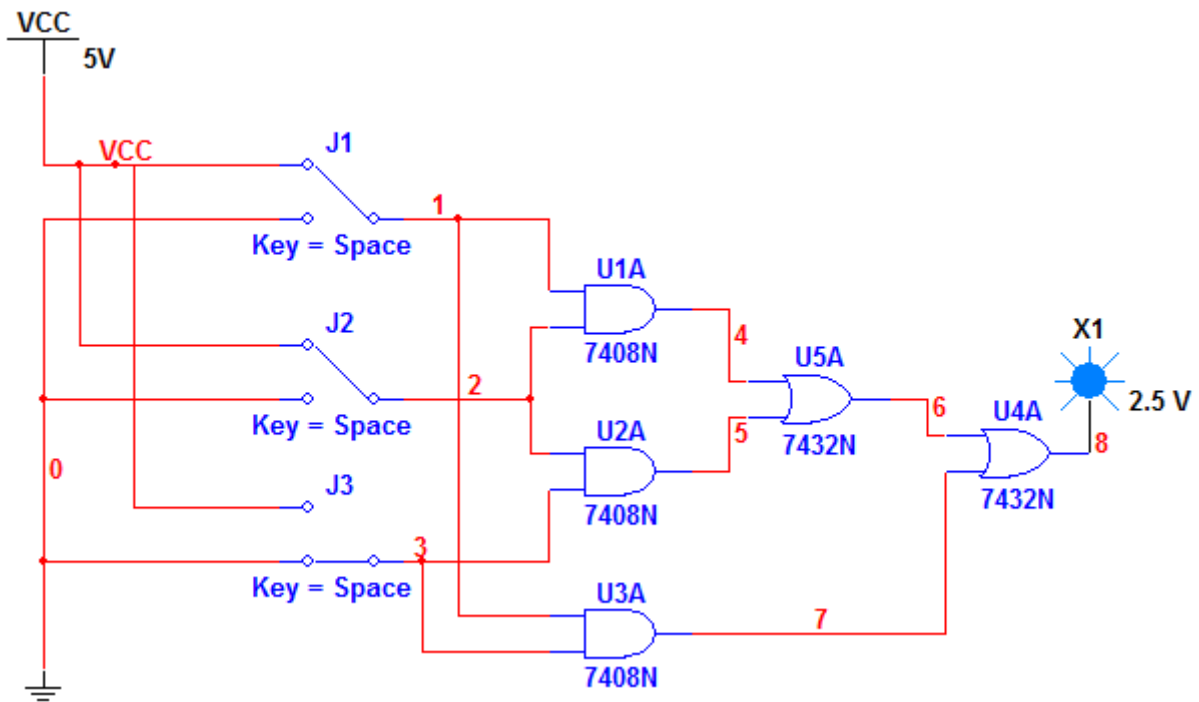

3. Let variables T represent being tall, H being heavy and F being fast. Let's consider anyone who is not tall (T') as short, not heavy as light and not fast as slow. Write a Boolean equation to represent the following:

You may ride (represented by R) a particular amusement park ride only if you are either tall and light, or short and heavy and fast.

Truth Table:


T	H	F	R
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Expression:

$$R(T,H,F)=m(3,4,5)$$

$$R=TH'+T'HF$$

Multi Sim Circuit Diagram:

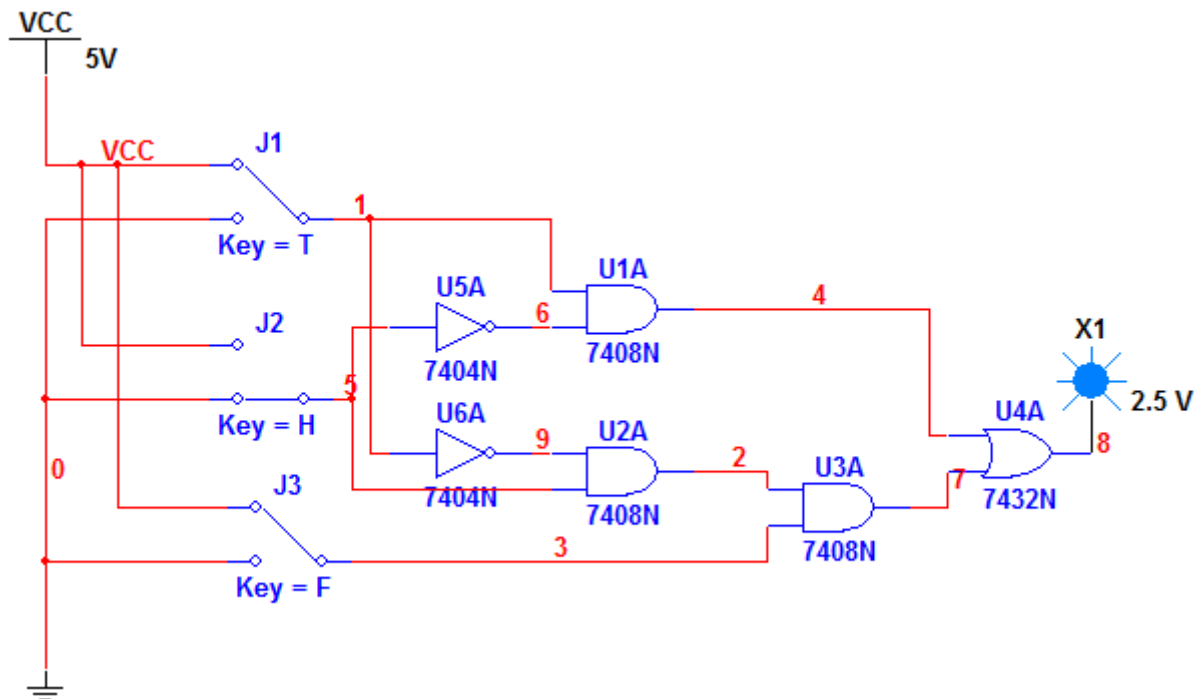

HARDWARE:

Q.3

H/w verified

Expt. No. Date

Page No. 12

Q.3

$T = \text{Tall}$
 $H = \text{Heavy}$
 $F = \text{Fast}$

3 input

$R = \text{Allowed}$
 on ride

1 output

T	H	F	R
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$R(T, H, F) = \sum m(3, 4, 5)$

$R = T\bar{H} + \bar{T}HF$

T

00
01
11
10

0	1	1	1
1	1	1	1

X

Teacher's Signature :

